



Istanbul Technical University
Department of Computer Engineering

14.10.2016

BLG 231E - Digital Circuits Assignment 2

Due Date: 20.10.2016, **Thursday**, 17.00.

- Please **write neatly**.
- If you are not preparing your homework in a computer, please show complement of a symbol by putting a **dash** over the symbol (e.g. do not use x' use \bar{x}).
- **Consequences of plagiarism:** Disciplinary regulations of The Council of Higher Education and of the university are applied.
- **No late submissions** will be accepted.

Submissions: Please submit your solutions to the Digital Circuits Course Assignment Box at the department secretary's office.

f and g are two logical functions, where

$$f(a, b, c, d) = \sum m(0, 2, 3, 7, 8, 10, 12, 13),$$

$$f(a, b, c, d) + g(a, b, c, d) = \prod M(1, 4, 6, 14), \text{ and}$$

$$f(a, b, c, d) \cdot g(a, b, c, d) = \sum m(7, 13).$$

- Write the first and the second canonical forms for the function $g(a, b, c, d)$.
- Minimize the logical expression for g in SoP (*sum of products*) form.
- Design and draw the circuit for the expression found in **ii** using only **2-input NOR gates**.