



Istanbul Technical University  
Department of Computer Engineering

04.11.2016

## BLG 231E - Digital Circuits Assignment 3

**Due Date:** 14.11.2016, **Monday**, 17.00.

- Please **write neatly**.
- If you are not preparing your homework in a computer, please show complement of a symbol by putting a **dash** over the symbol (e.g. do not use  $x'$  use  $\bar{x}$ ).
- **Consequences of plagiarism:** Disciplinary regulations of The Council of Higher Education and of the university are applied.
- **No late submissions** will be accepted.

### **Submissions:**

- Please submit your solutions on a paper to the Digital Circuits Course Assignment Box at the department secretary's office (set of all prime implicants, prime implicant chart and simplification)
- Additionally, submit the circuit implemented with the simulation program (\*.circ file) to Ninova.

---

1. Find **all** prime implicants of the following **incomplete** function by using Karnaugh Maps.

$$f(a, b, c, d) = \bigcup_1 (0, 4, 5, 9, 12, 14) + \bigcup_0 (6, 7, 11, 13, 15)$$

2. Create the prime implicant chart according to the given cost criteria and simplify it. Explain **each** step of the simplification. Write the expression of the function with the least cost and give the total cost.

**Cost criteria:** 2 units for each variable and 1 unit for each complement.

3. Implement the expression that you obtained in the question 2 using only two-input **NOR** gates. Do not use unnecessary gates.

4. Realize the circuit you have designed in the question 3 by using the digital circuit simulator "**logisim**". Explain the reasons for the output values generated by the input combinations in the set  $\cup_{\Phi}$  (*Undetermined/do not care values*).

**Reminder:** You should **submit** your design (\*.circ file) through Ninova e-learning system.

You could download **logisim** from the link given below:

<http://www.cburch.com/logisim/download.html>