

Lecture 2

Memory Card with 8 Chips


- Each chip is 16 M x 1 b (16 mega bits)
- Card total is 16 M x 8 b (16 mega byte)
- We can install several memory card modules on the main board of computer.



DATA BUS / ADDRESS BUS / CONTROL BUS

 Example : 3-to-8 Decoder

- There are 3 inputs, and $2^3 = 8$ output lines.
- Depending on the inputs, only one of the output lines will be 1, all other output lines will be 0.






Truth Table for 3-to-8 Decoder

- Only one output line is selected at a time.

INPUTS			OUTPUTS							
A ₂	A ₁	A ₀	L ₇	L ₆	L ₅	L ₄	L ₃	L ₂	L ₁	L ₀
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0


Inside of 3-to-8 Decoder

   - Decoders are manufactured as standard Integrated Circuits.




Logic Gates and their Electronic Circuit Implementation


NOR Gate

 

 NOR Gate Circuit RTL (Resistor Transistor Logic)




AND Gate Circuit

 

Multiplexer, Demultiplexer, Decoder

MULTIPLEXER

 
Only one of the Inputs is selected, and it is forwarded to the output.



DEMULTIPLEXER

Only one of the Outputs is selected, and the input is forwarded to it.

 If Input is constantly "1", this is a DECODER.




Simplest Example: 1-to-2 line decoder

A is the address and D is the selected lines.

D₀ is NOT A. ($D_0 = A'$)

D₁ is A ($D_1 = A$)

Circuit (Inverter)

 


Truth Table

A	D ₁	D ₀
0	0	1
1	1	0

Example: 2-to-4 line decoder


Circuit (Inverters + And gates)

 

Truth Table

A_1	A_0	D_3	D_2	D_1	D_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

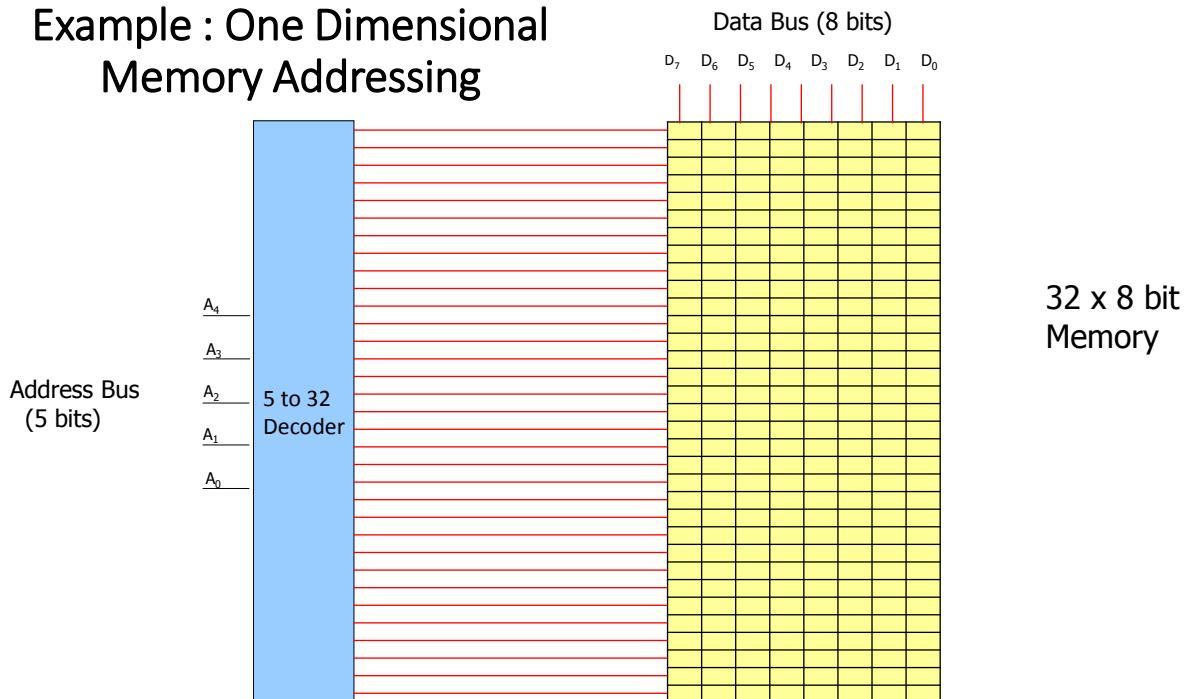Example : One Dimensional Memory Addressing



Some Terminology

- **COMBINATIONAL CIRCUIT**
 - Outputs depend only on the current inputs.
- **SEQUENTIAL CIRCUIT**
 - Outputs depend both on the inputs and the state of circuit (previous outputs).
 - Memory units must be Sequential circuits.
- **FLIP-FLOP** is a memory unit that is triggered by a clock signal.
- **LATCH** is a memory unit that is not triggered by a clock signal.
 - The value of latch can be changed whenever the latch is enabled.
- **CACHE** is a memory faster than RAM.
 - Stores frequently used instructions and data.
 - Primary cache (Level1): Located within the CPU.
 - Secondary cache (Level2): Located near the CPU.

Example Metrics of Memory

Memory Type	Capacity	Access Time
Registers in CPU	1 KB	1 ns
Caches in CPU	1 MB	10 ns
Main Memory (RAM)	10 GB	100 ns
Hard Disk Drive	1 TB	10 ms

Metrics used for Memory

1 Byte = 8 bits (Binary DigiT)

Unit	Name	Synonym	Real Value (base 2)	Approximate Value (base 10)
1 KB	Kilo	Thousand	$2^{10} = 1024$	$10^3 = 1000$
1 MB	Mega	Million	2^{20}	10^6
1 GB	Giga	Billion	2^{30}	10^9
1 TB	Tera	Trillion	2^{40}	10^{12}

Metrics used for CPU speed

Hertz (clock rate) is the unit of frequency measurement.

It represents number of clock cycles (of periodic pulse wave) **per second**.

Frequency Unit	Unit name	Synonym	Hertz Value
1 KHz	Kilo	Thousand	10^3
1 MHz	Mega	Million	10^6
1 GHz	Giga	Billion	10^9
1 THz	Tera	Trillion	10^{12}

Time Unit	Unit name	Synonym	Seconds Value
1 ms	Mili	One thousandth of a second.	10^{-3}
1 μ s	Micro	One millionth	10^{-6}
1 ns	Nano	One billionth	10^{-9}
1 ps	Pico	One trillionth	10^{-12}

Example : CPU Clock Period

Assume the CPU clock frequency is 100 MHz.


QUESTION: Find the pulse wave period in terms of nano seconds.

$$\text{Period (seconds)} = \frac{1}{\text{Frequency}}$$

$$= \frac{1}{100 \times 10^6} = 10^{-8} \text{ seconds}$$

$$= 10^{-8} \text{ seconds} \times 10^9 \text{ nanoseconds/second}$$

$$= 10 \text{ nanoseconds}$$

 

SRAM versus DRAM


Memory Type	Number of bits in a chip	Speed	Where used
SRAM (Static)	8	Fast	Cache
DRAM (Dynamic)	1	Slow	Main memory

Lecture 3

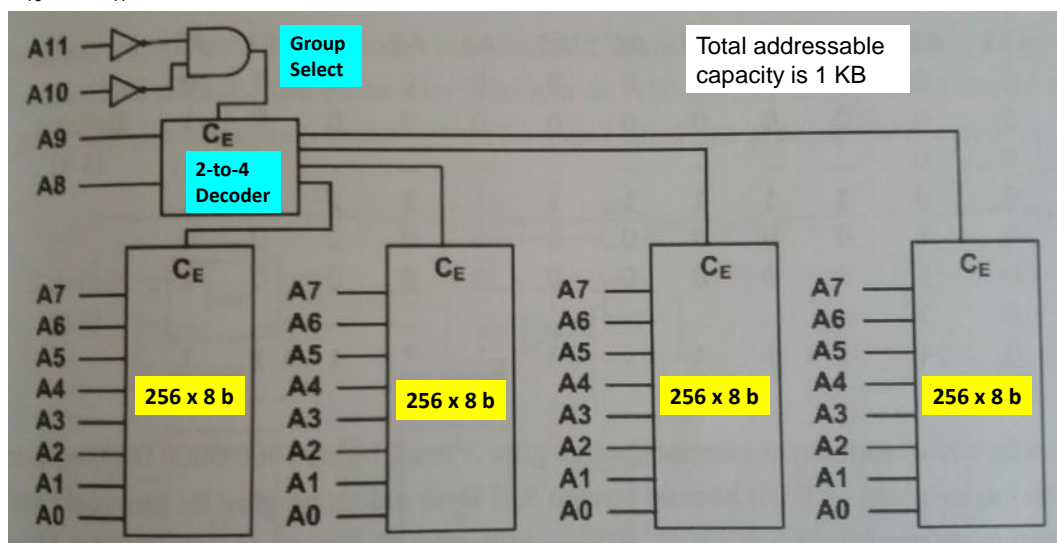Example 1 : Memory Design

- Data Bus = 8 bits, Address Bus = 12 bits
- Each memory chip is 256 x 8 bits.
- A_0 through A_7 used for location selection inside a chip ($2^8 = 256$ rows)
- Decoder used for chip selections (C_E : Chip enable)
- A_{10} and A_{11} used to select the decoder itself.

For simplicity, Data Bus and R/W ' is ignored.



Memory Address Map

MEMORY CHIP	DECODER SELECT		CHIP SELECT		LOCATION SELECTION WITHIN A CHIP							
	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
MEMORY 1	0	0	0	0	0	0	0	0	0	0	0	0
	0	0	0	0	0	0	0	0	0	0	0	1
	0	0	0	0
	0	0	0	0	1	1	1	1	1	1	1	1
MEMORY 2	0	0	0	1	0	0	0	0	0	0	0	0
	0	0	0	1	0	0	0	0	0	0	0	1
	0	0	0	1
	0	0	0	1	1	1	1	1	1	1	1	1
MEMORY 3	0	0	1	0	0	0	0	0	0	0	0	0
	0	0	1	0	0	0	0	0	0	0	0	1
	0	0	1	0
	0	0	1	0	1	1	1	1	1	1	1	1
MEMORY 4	0	0	1	1	0	0	0	0	0	0	0	0
	0	0	1	1	0	0	0	0	0	0	0	1
	0	0	1	1
	0	0	1	1	1	1	1	1	1	1	1	1

Memory Address Map (Binary and Hexadecimal)


CHIP	SMALLEST ADDRESS												BIGGEST ADDRESS											
	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
M1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
M2	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1
M3	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	1	1	1	1	1	1
M4	0	0	1	1	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1
GAP	0	1	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1

- Total possible capacity is $2^{12} = 4 \text{ KB}$
- Addressable capacity is 1 KB.
- The last 3 KB is unused gap space.
- Addresses 400 thru FFF are undefined (unaccessible) !

CHIP	SMALLEST ADDRESS (A ₁₁ – A ₀)	BIGGEST ADDRESS (A ₁₁ – A ₀)	CAPACITY
M1	0 0 0	0 F F	256 B
M2	1 0 0	1 F F	256 B
M3	2 0 0	2 F F	256 B
M4	3 0 0	3 F F	256 B
GAP	4 0 0	F F F	3 KB

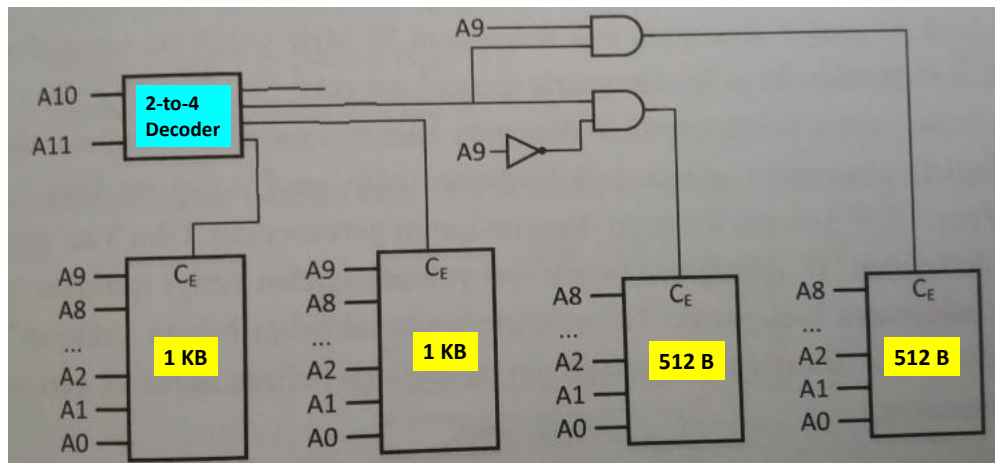Example 2 : Memory Design with different chips

- Total addressable capacity is $= (1 \text{ KB} * 2) + (512 \text{ B} * 2) = 3 \text{ KB}$



Memory Address Map (Binary and Hexadecimal)


CHIP	SMALLEST ADDRESS												BIGGEST ADDRESS											
	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
M1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1
M2	0	1	0	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1
M3	1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	1	1	1	1	1	1	1	1	1
M4	1	0	1	0	0	0	0	0	0	0	0	0	1	0	1	1	1	1	1	1	1	1	1	1
EMPTY	1	1	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1

- Total possible capacity is $2^{12} = 4 \text{ KB}$
- Addressable capacity is 3 KB.
- The last 1 KB is unused gap space.

CHIP	SMALLEST ADDRESS (A ₁₁ – A ₀)	BIGGEST ADDRESS (A ₁₁ – A ₀)	CAPACITY
M1	0 0 0	3 F F	1 KB
M2	4 0 0	7 F F	1 KB
M3	8 0 0	9 F F	512 B
M4	A 0 0	B F F	512 B
GAP	C 0 0	F F F	1 KB

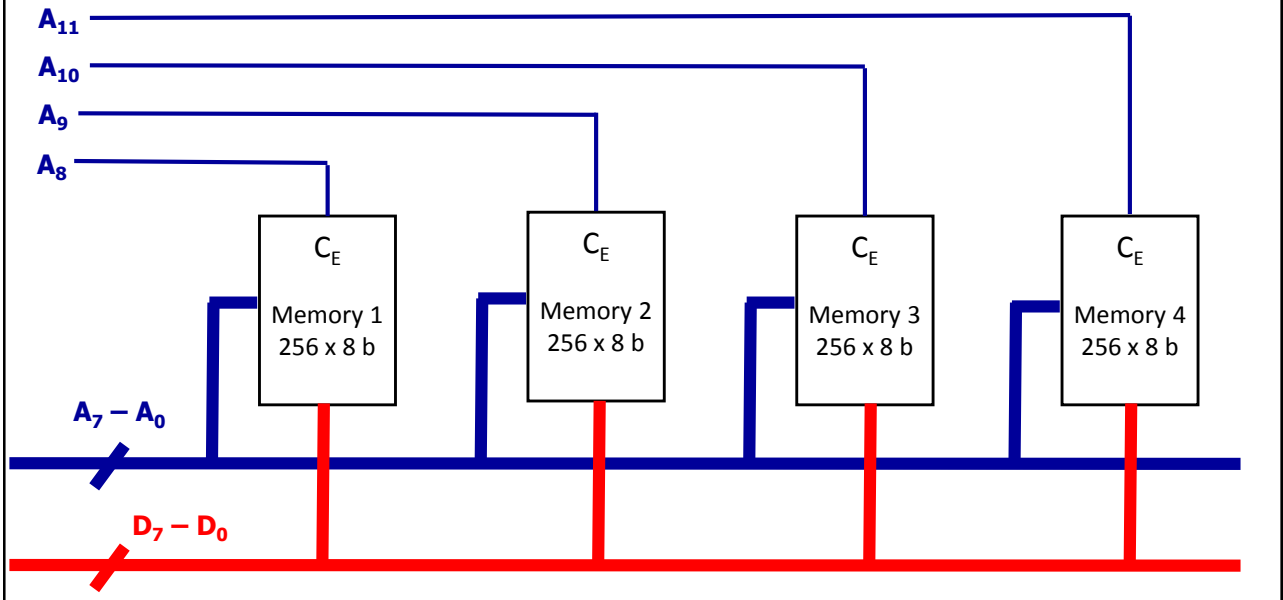Example 3 : Memory Design without Address Decoder

- Total addressable capacity is $= 2^8 \times 4 = 256 \text{ B} \times 4 = 1 \text{ KB}$



Memory Address Map (Binary and Hexadecimal)

CHIP	SMALLEST ADDRESS												BIGGEST ADDRESS											
	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
M1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1
M2	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1	1	1	1	1	1	1
M3	0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	1	1	1	1	1	1	1	1
M4	1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	1	1	1	1	1	1	1	1
EMPTY	0	1	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1

- Total possible capacity is $2^{12} = 4 \text{ KB}$
- Addressable capacity is 1 KB.

- Total unused gap space = $12 \times 256 \text{ B} = 3 \text{ KB}$
(IRREGULARLY SPACED !)

CHIP	SMALLEST ADDRESS (A ₁₁ - A ₀)	BIGGEST ADDRESS (A ₁₁ - A ₀)	CAPACITY
GAP	0 0 0	0 F F	1 x 256 B
M1	1 0 0	1 F F	256 B
M2	2 0 0	2 F F	256 B
GAP	3 0 0	3 F F	1 x 256 B
M3	4 0 0	4 F F	256 B
GAP	5 0 0	7 F F	3 x 256 B
M4	8 0 0	8 F F	256 B
GAP	9 0 0	F F F	7 x 256 B

Calculation of unused (gaps) address bytes

Smallest Address	Biggest Address	Count of Bytes
0 0 0	0 F F	256

Smallest Address	Biggest Address	Count of Bytes
3 0 0	3 F F	256

Smallest Address	Biggest Address	Count of Bytes
5 0 0	5 F F	256
6 0 0	6 F F	256
7 0 0	7 F F	256

Smallest Address	Biggest Address	Count of Bytes
9 0 0	9 F F	256
A 0 0	A F F	256
B 0 0	B F F	256
C 0 0	C F F	256
D 0 0	D F F	256
E 0 0	E F F	256
F 0 0	F F F	256

Total unused gap space
 $12 \times 256 \text{ B} = 3 \text{ KB}$

Disadvantage of not using a decoder

- If an address decoder is not used, utilization of address bus will be ineffective.
- The possible addresses of memory with a 12-bit Address Bus is $2^{12} = 4 \text{ KB}$.
- Without using a decoder, 4 bits are used for chip selection, 8 bits are used for location selection within chips.
- Therefore addressable memory is $4 \times 2^8 = 1 \text{ KB}$.
- The unused gap 3 KB is a waste of space capacity.


Mirroring Problem

- If a decoder is not used, or decoder is used but a decoder selection circuit (group selection) is not used, there is a possibility of mirroring.
- If an invalid address (in gap) is used by programmer, more than one memory chip can be selected at the same time. (This is known as **Mirroring problem**.)
- For example: The Address **F00** will select all of the 4 memory chips.
(In fact, any FXX address will always select all chips at the same time.)
- Mirroring causes **system deadlock**.


Example Address	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
F 0 0	1	1	1	1	0	0	0	0	0	0	0	0

SELECTED CHIPS	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
M1	0	0	0	1	0	0	0	0	0	0	0	0
M2	0	0	1	0	0	0	0	0	0	0	0	0
M3	0	1	0	0	0	0	0	0	0	0	0	0
M4	1	0	0	0	0	0	0	0	0	0	0	0

 Solving the Mirroring Problem with AND Gates



 Solving the Mirroring Problem with AND Gates



- Normally, an address decoder should be preferred for chip selections.
- This is just an example of alternative solution.

Lecture 4

Sequential Processing

Sequential processing works on one instruction at a time

Cycle	1	2	3	4	5	6	7	8	9
Instr ₁	Fetch	Decode	Execute	Write					
Instr ₂					Fetch	Decode	Execute	Write	
Instr ₃									Fetch

Pipelined Processing

Cycle	1	2	3	4	5	6	7	8	9
Instr ₁	Fetch	Decode	Execute	Write					
Instr ₂		Fetch	Decode	Execute	Write				
Instr ₃			Fetch	Decode	Execute	Write			
Instr ₄				Fetch	Decode	Execute	Write		
Instr ₅					Fetch	Decode	Execute	Write	
Instr ₆						Fetch	Decode	Execute	Write

- Latency — elapsed time from start to completion of a particular task
- Throughput — how many tasks can be completed per unit of time
- Pipelining only improves throughput
 - Each job still takes 4 cycles to complete
- Analogy: Factory assembly line