

$$1) a) ff = \frac{X_{ef}}{X_{m_{abs}}} \rightarrow ff^* = \frac{X_{ef}/\sqrt{2}}{X_{m_{abs}}/2} = \sqrt{2} \cdot ff = \underline{\underline{\sqrt{2} \cdot 1,15}}$$

$$b) U_{m_{abs}} = \frac{U_m \cdot t_1/2}{2t_1} = \frac{U_m}{4} \rightarrow U = \underline{\underline{\frac{U_m}{4} \cdot 1,15}}$$

16.04.2013


Measurement & Instrumentation

Midterm Exam

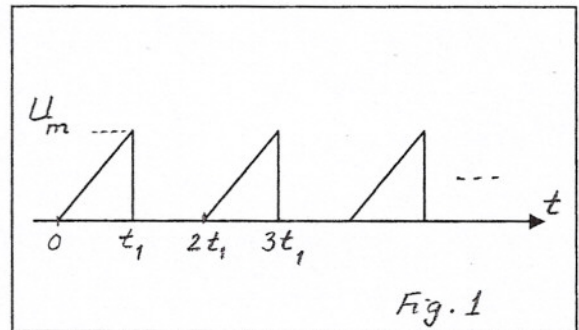1) The form factor of a triangle wave is 1,15. According to this information,

20 a) Calculate the form factor of the signal in Fig.1

20 b) Which value does a full-wave rectifier instrument read for this signal? (Calculate the reading in terms of U_m).



25 2) A magnitude 'x' is calculated as $x = a + b/c^2$, where

'a' is given as $a = 10.0$ [u] with its significant numbers,

'b' is given as $b = 5 \pm 0.03$ [u]

'c' is given as $c = 5$ [u], 1%

$$\begin{aligned} \Delta x &= \Delta a + \frac{1}{c^2} \cdot \Delta b + \frac{2b}{c^3} \cdot \Delta c \\ &= 0,05 + \frac{1}{25} \cdot 0,03 + \frac{10}{125} \cdot 0,05 \\ &= 0,0552 \end{aligned}$$

Calculate the relative error in evaluating 'x'.

$$\frac{\Delta x}{x} = \frac{0,0552}{10,2} = \underline{\underline{\% 0,54}}$$

3) In Fig.2

Z_1 is an inductive load of 100Ω , $\cos \varphi_1 = 0.8$.

Z_2 is an inductive load of 100Ω .

W-m : 300V, 5A, 60 div., $R_{aw} = 10 \text{ m}\Omega$, $R_{vw} = 100 \text{ k}\Omega$

30 a) Calculate the power factor of Z_2 , if the wattmeter deflects by 30 divisions.

15 b) Calculate the relative method error in power measurement.

$$a) P_{tot} = P_{Z_1} + P_{Z_2} = \frac{300 \cdot 5}{60} \cdot 30 = 750 \text{ W}$$

$$P_{Z_1} = \frac{220^2}{100} \cdot 0,8 = 387,2 \text{ W}$$

$$P_{Z_2} = 362,8 \text{ W}$$

$$= \frac{220^2}{100} \cdot \cos \varphi_2$$

$$\cos \varphi_2 \approx 0,75$$

$$b) \Delta P|_{\text{met.}} = \frac{220^2}{R_{vw}} \approx 0,5 \text{ W}$$

$$\left| \frac{\Delta P}{P} \right|_{\text{met.}} \approx 0,06 \%$$

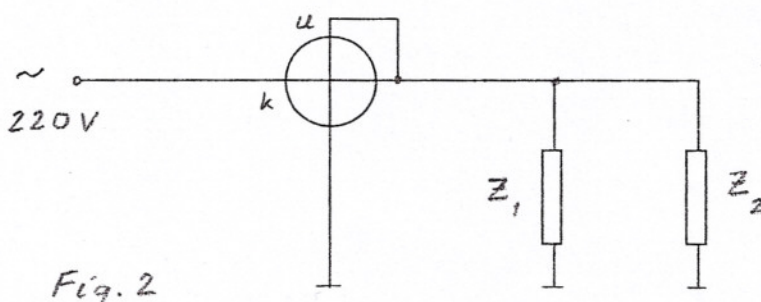


Fig. 2

110 p.

Measurement & Instrumentation

Midterm Exam

- 1) Given the voltage

$$U_{m_{abs}} = 1, U_{ef} = \sqrt{1^2 + \left(\frac{a}{\sqrt{2}}\right)^2} \rightarrow ff = \frac{U_{ef}}{U_{m_{abs}}} = 1,2 \rightarrow \alpha \approx 0,94$$

$$u(t) = 1 - a \cdot \cos(\omega t - \pi/6) \text{ [V] with } a < 1.$$

- 20 a) Calculate 'a' if the form factor of u(t) is ff=1,2.

- 15 b) Which value does a full-wave rectifier instrument (V-m) read for this input voltage?

$$U_{fwr} = U_{m_{abs}} \cdot 1,11 = 1,11 \text{ V}$$

- 2) In Fig. 2:

$u(t) = 10 \cdot \cos(\omega t) \text{ [V]}$, $R = 10 \Omega$. The measuring instruments and the diodes are considered to be ideal. Which value does

- 15 a) the moving-coil Ammeter

$$I_m = \frac{0,5}{\pi} = 0,16 \text{ A}$$

- 15 b) the moving-iron V-meter read?

$$U_{ef} = \frac{5}{2} = 2,5 \text{ V}$$

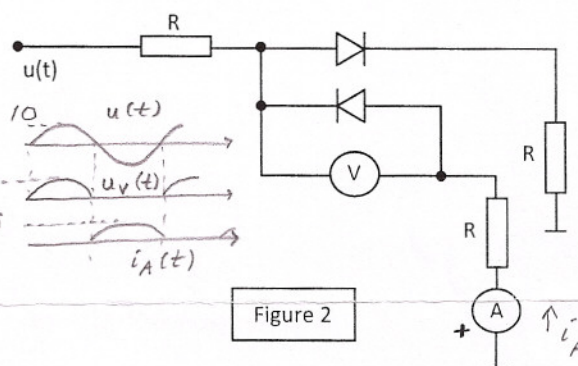


Figure 2

- 3) In Fig.3 the instruments have the following characteristics:

Wh-m: 220V, 10A, 750rev/kWh

W-m: 250V, 10A, 50div., $cl_w = 0.5$

A-m: 3A, 30div., $cl_A = 1$

Current transformer CT1: 25A/5A, $cl_{ct1} = 0.2$

Current transformer CT2: 10A/5A, $cl_{ct2} = 0.2$

The W-m deflects by 30 divisions and the Ammeter reads 2A.

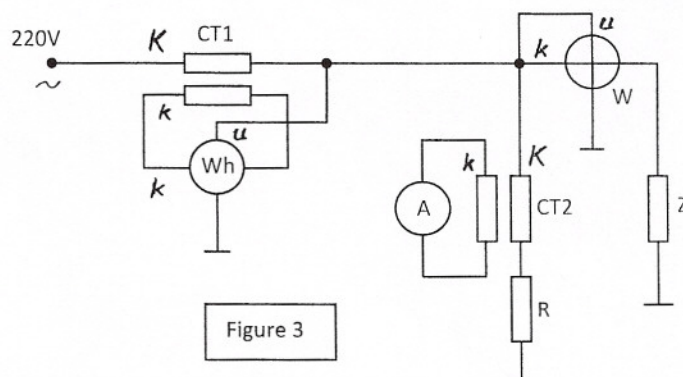


Figure 3

- 20 a) Calculate the total power (
- P_{tot}
-) drawn by the loads.

- 20 b) Evaluate the instrumental error in calculating
- P_{tot}
- .

- 15 c) How long does it take for the electromechanical Wh-meter to complete 20 revolutions?

120 p.

$$a) P_z = P_w = \frac{250 \cdot 10}{50} \cdot 30 = 1500 \text{ W}, P_R = (k_{I_z} \cdot I_A)^2 \cdot R = U \cdot I_R = 220 \cdot 4 = 880 \text{ W}$$

$$P_{tot} = 2380 \text{ W}$$

$$b) \Delta P_{tot} = \Delta P_z + \Delta P_R = \%0,5 \cdot 2500 + \left(\%1 \cdot \frac{3}{2} + \%0,2 \right) \cdot 880$$

$$= 27,46 \text{ W} \rightarrow \frac{\Delta P_{tot}}{P_{tot}} = 1,15\%$$

$$c) t = \frac{3600 \cdot 20}{750 \cdot \frac{2380}{5}}, 20 \approx 201,7 \text{ sec.}$$