Microprocessor SystemsFinal Exam

1- Calculate the value of A (Accumulator) by using hexadecimal number system at the end of logical and arithmetic operations listed below.

a) MOV A,#50D MOV R0,A LOOP: ADD A,R0 DJNZ R0,LOOP A=(?)₁₆

MOV 30H,#0FH MOV R0,#2FH XRL 30H,#0D0H INC R0 MOV A,@R0

 $A=(?)_{16}$

- 2- 12MHz crystal is connected to a 89C52 microcontroller (8x51 family member). Write a program that generates 80Hz (%50Duty cycle) periodic signal at the port pin P1.0. Crystal frequency division rate of the microcontroller is 1/12 and interrupt address of the Timer 0 is 0BH. (Main program loop must be independent from 80Hz signal generation)
- 3- An 8 bit CPU having 64KBytes addressing capability will be connected to a memory block that is consisting of 1 piece of 27C256 EPROM, 1 piece of 62C64 static RAM, 2 pieces of 74HC573 (8 bits single directional latch) and an address decoder unit. 4 relays and 4 pieces of seven segments+deep point type, common cathode LED display will be driven through the outputs of the 74HC573. Relays will be driven through NPN transistors. Reset vector assigns ProgramCounter=0000H.
- a) Draw the memory-addressing map of the described system and related logical chip selection table for the decoder.
- b) Draw the circuit schema of the system using 74HC138 as the decoder IC. (Value of the components may not be calculated)
- c) Components' electrical parameters are given as,

LED Display: I_{AC} =8mA/segment (static), V_{AC} =1.2V

NPN transistor: hFE=400, V_{BE}=0.7, V_{CEsat}=0.2V

PNP transistor: hFE=200, V_{BE}=0.7, V_{CEsat}=0.3V

Relay: I_R≅100mA @ 5V

 $74HC573 : V_{Lmax} = 0.5V, V_{Hmin} = 4.5V, I_{max} = 10mA$

Calculate the required resistor values for driving the relays and the display @70Hz.

P: 1-a) 15P b)10P 2- 25P 3- a) 15P b) 25P c)15P

D: 95minutes