
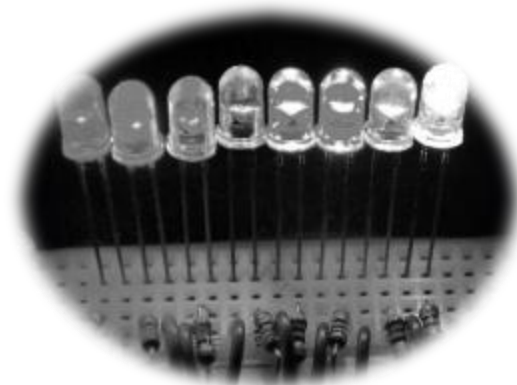
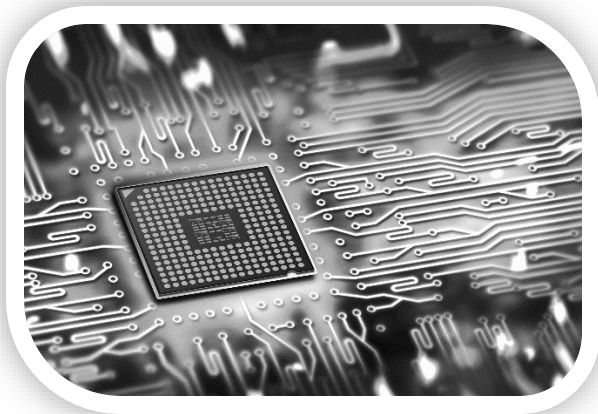


# Introduction to Electronics

## EHB222E

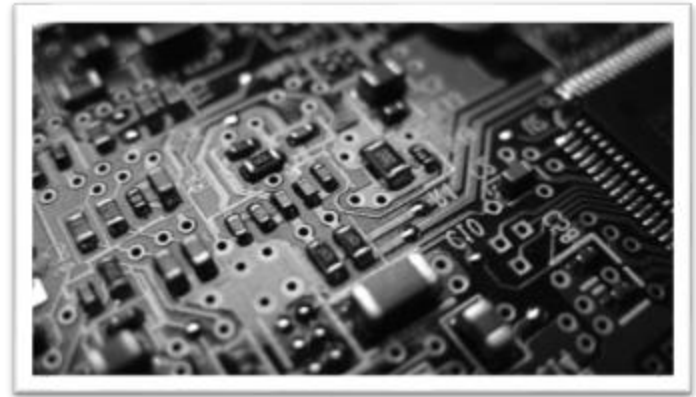


# Introduction to Electronics

- Introduction
- Semiconductors & Doping, Basics of pn junction
- Diodes
- BJT Transistors
- MOSFET Transistors
- Operational Amplifiers
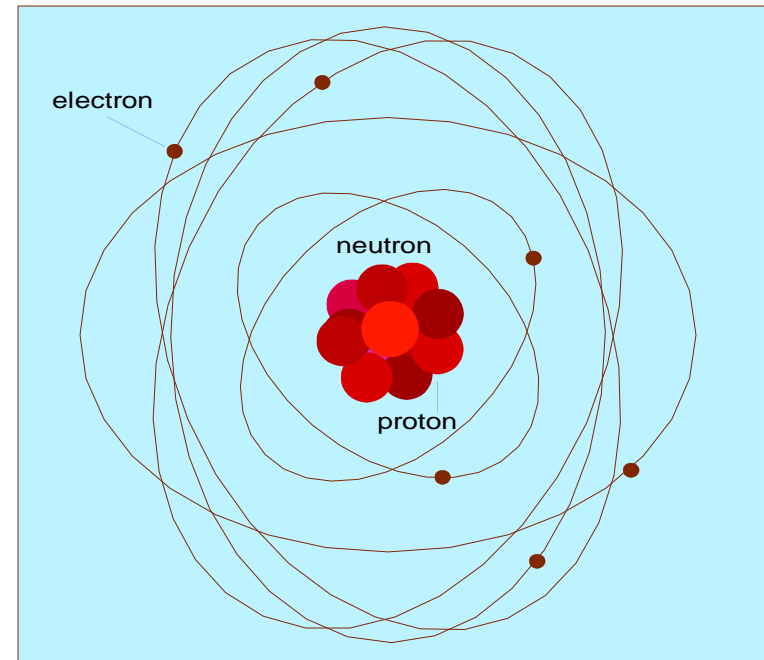
# What is Electricity?

- Electricity is generated from the **motion of tiny charged atomic particles** called electrons and protons!
- Protons = +
- Electrons = -



# What is Current?

- **When electrons** flows through a conductor
- We call this flow as "**current**."
- Only some materials have free electrons inside.

**YES!**

## Conductors:

silver  
copper  
gold  
aluminium  
iron  
steel  
brass  
bronze  
mercury  
graphite  
salty water

## Insulators:

**No free electrons = No  
current**


glass  
rubber  
oil

**NO!**

asphalt  
fiberglass  
porcelain  
ceramic  
quartz  
(dry) cotton  
(dry) paper  
(dry) wood  
plastic  
air  
diamond  
pure water
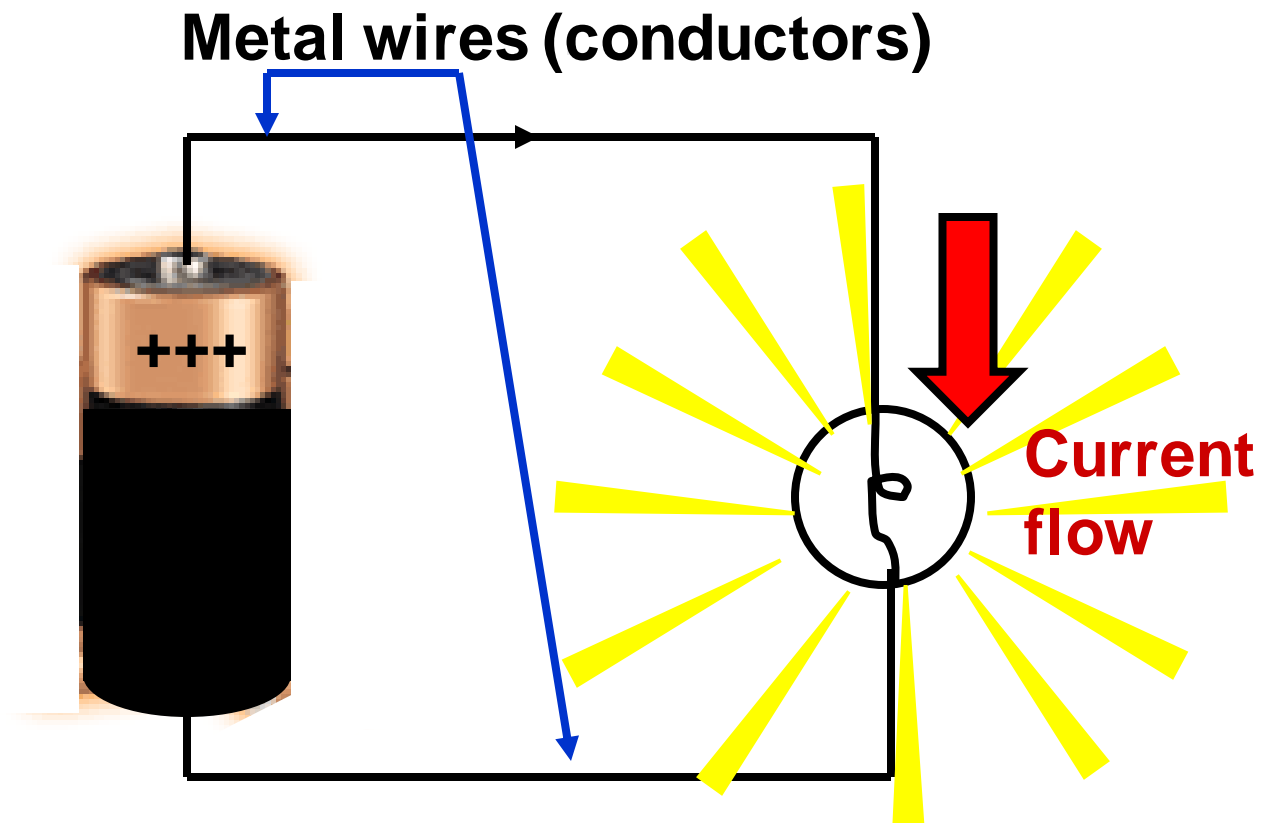
# How Does Current Flow?


Current can only flow through **conductors**



# When Does Current **NOT** Flow?


Current cannot flow through **insulators**

**Plastic material (insulators)**

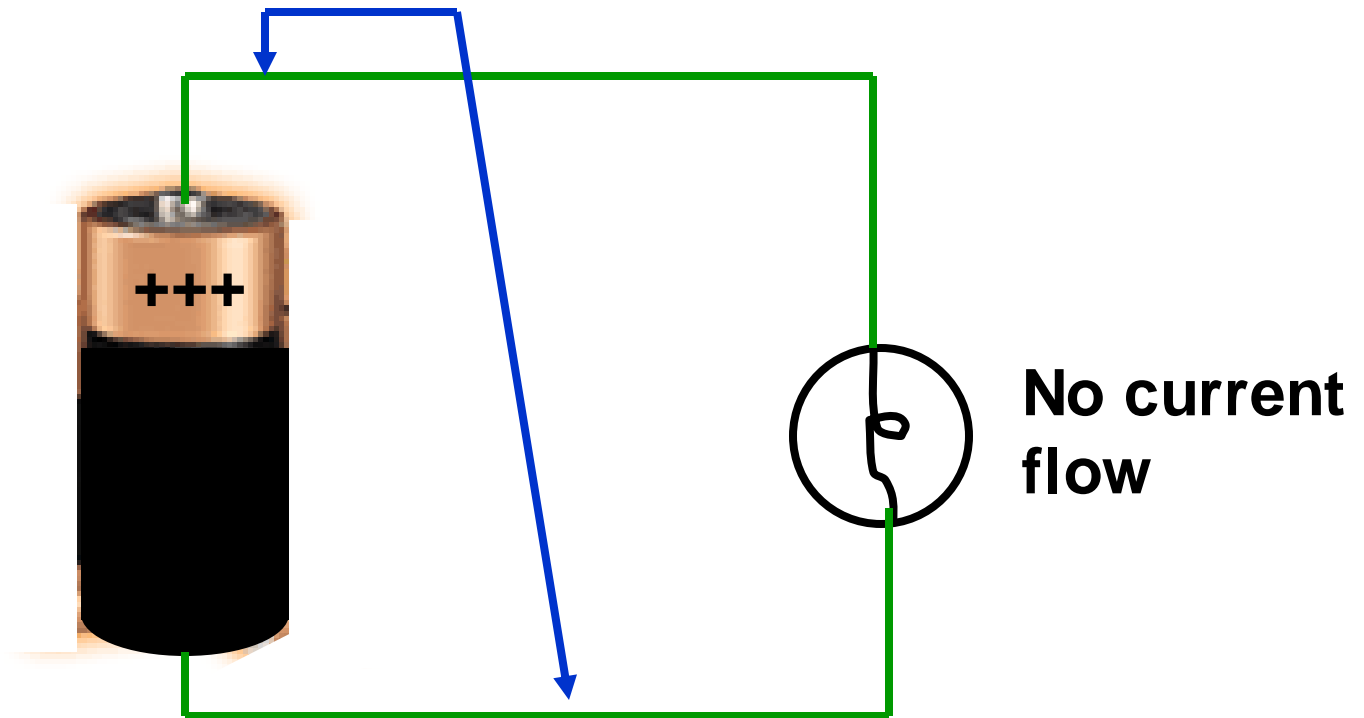
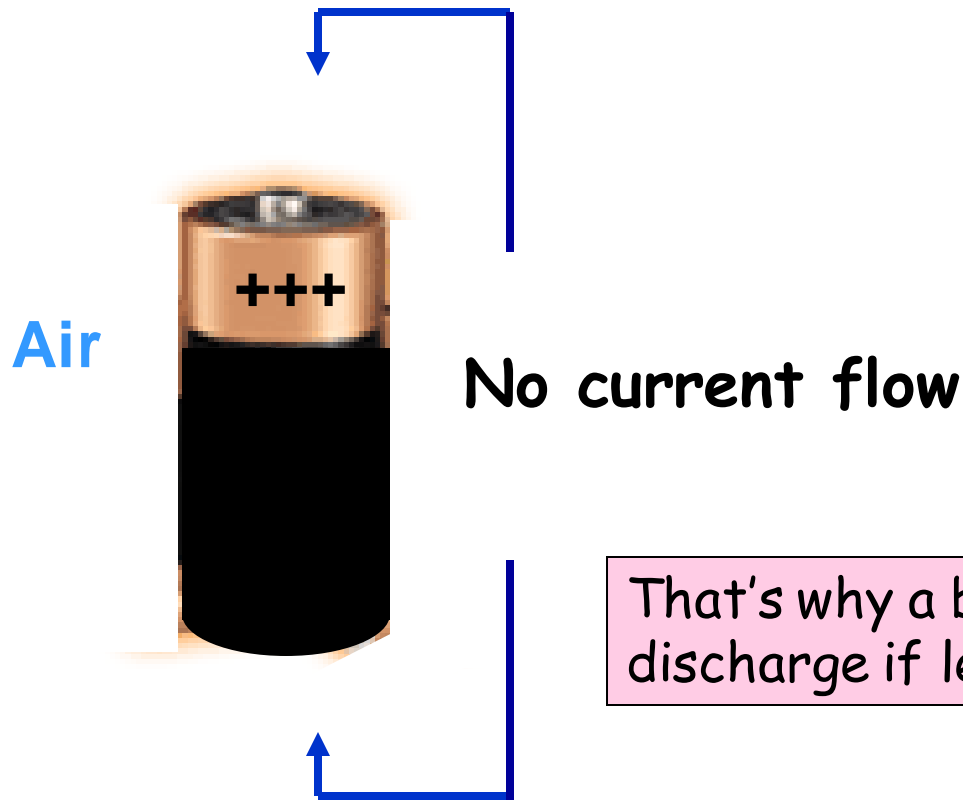
# Note that **Air** is an Insulator


Current cannot flow through **insulators**



That's why a battery doesn't discharge if left on its own.
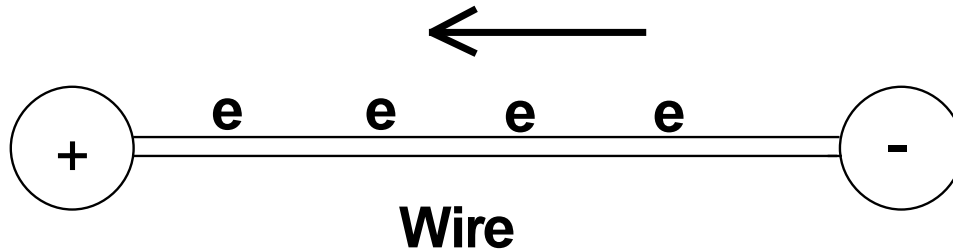
# Current


- Current is the amount of electric charge (coulombs) flowing past a specific point in a conductor over an interval of one second.  
 $1 \text{ ampere} = 1 \text{ coulomb/second}$
- Electron flow is from a lower potential (voltage) to a higher potential (voltage).




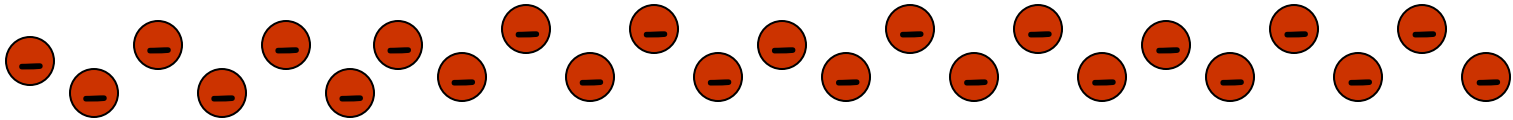
# Sign Convention for Current Flow

- Electrons carry negative charge
- Positive current flow is in opposite direction




electron motion

positive current direction


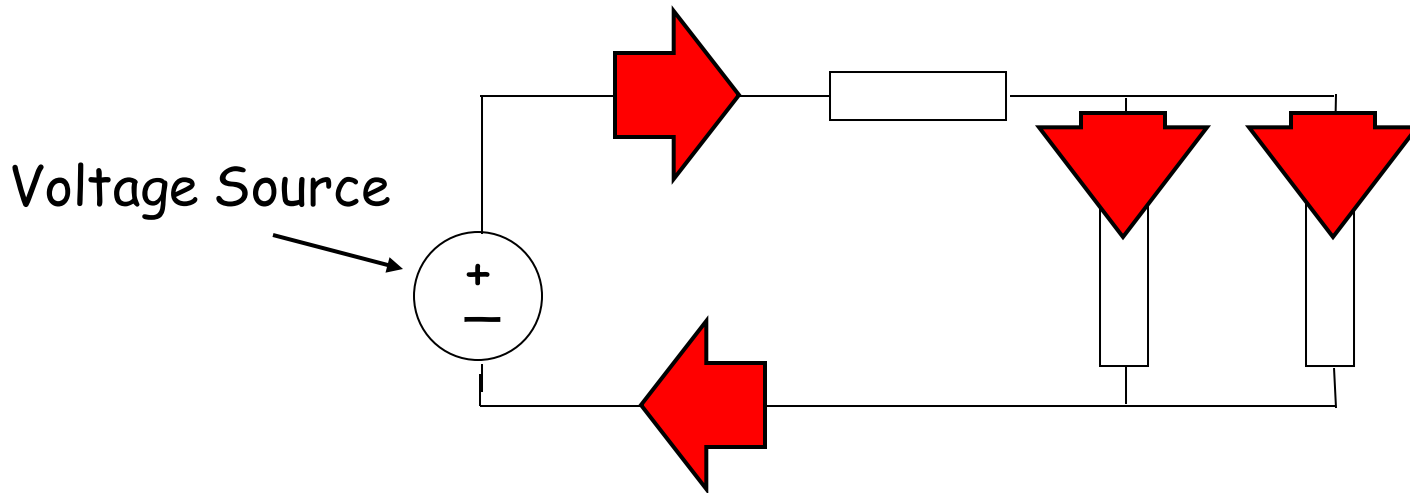
# Current Flow

- The **direction** of current flow is indicated by an arrow.




Note: The **voltage sources** in the circuit flow of current through nodes and wires.

# What is Voltage?


**Voltage is the difference in energy level** from one end of the battery (or any other energy source) to the other.

The **energy difference** causes the charges to move from a higher to lower voltage in a closed circuit

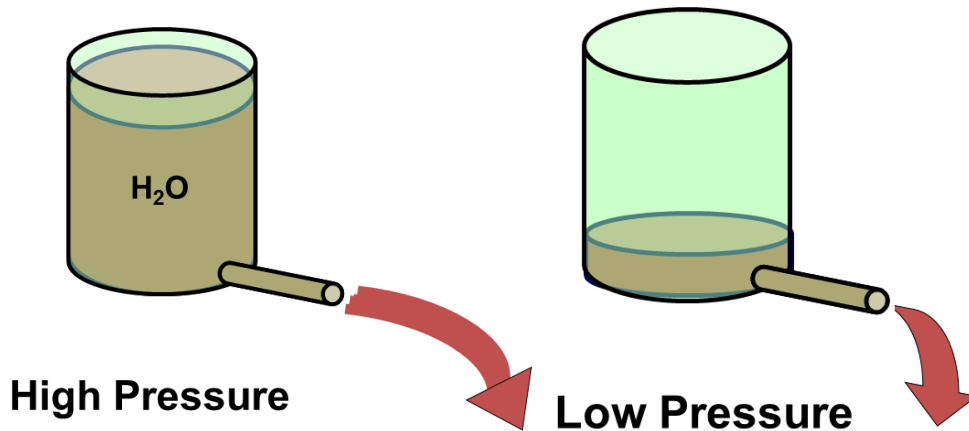$V$  = "Electrical pressure" - measured in **volts**.



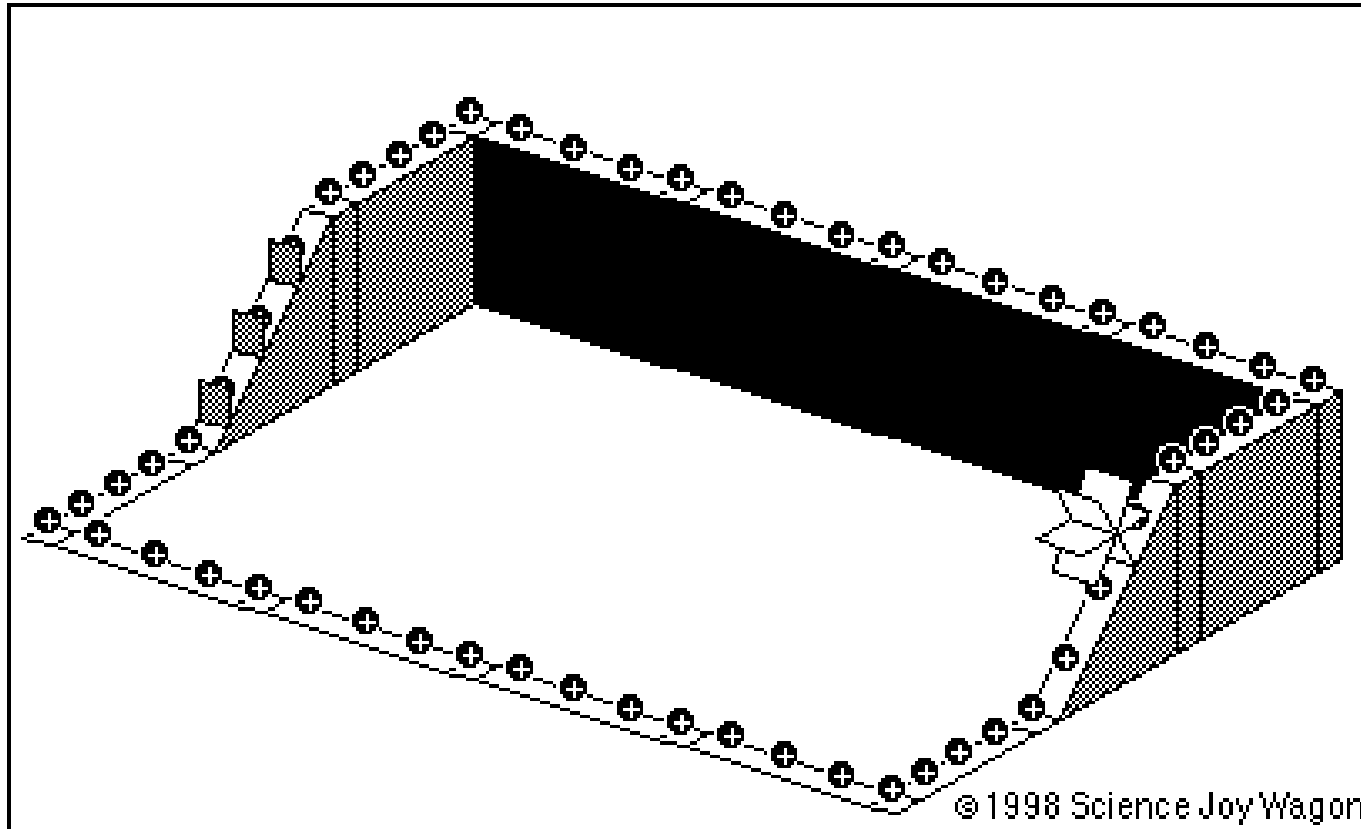
A battery in an electrical circuit plays the same role as a pump in a water system.



A battery establishes a difference of potential that can pump electrons


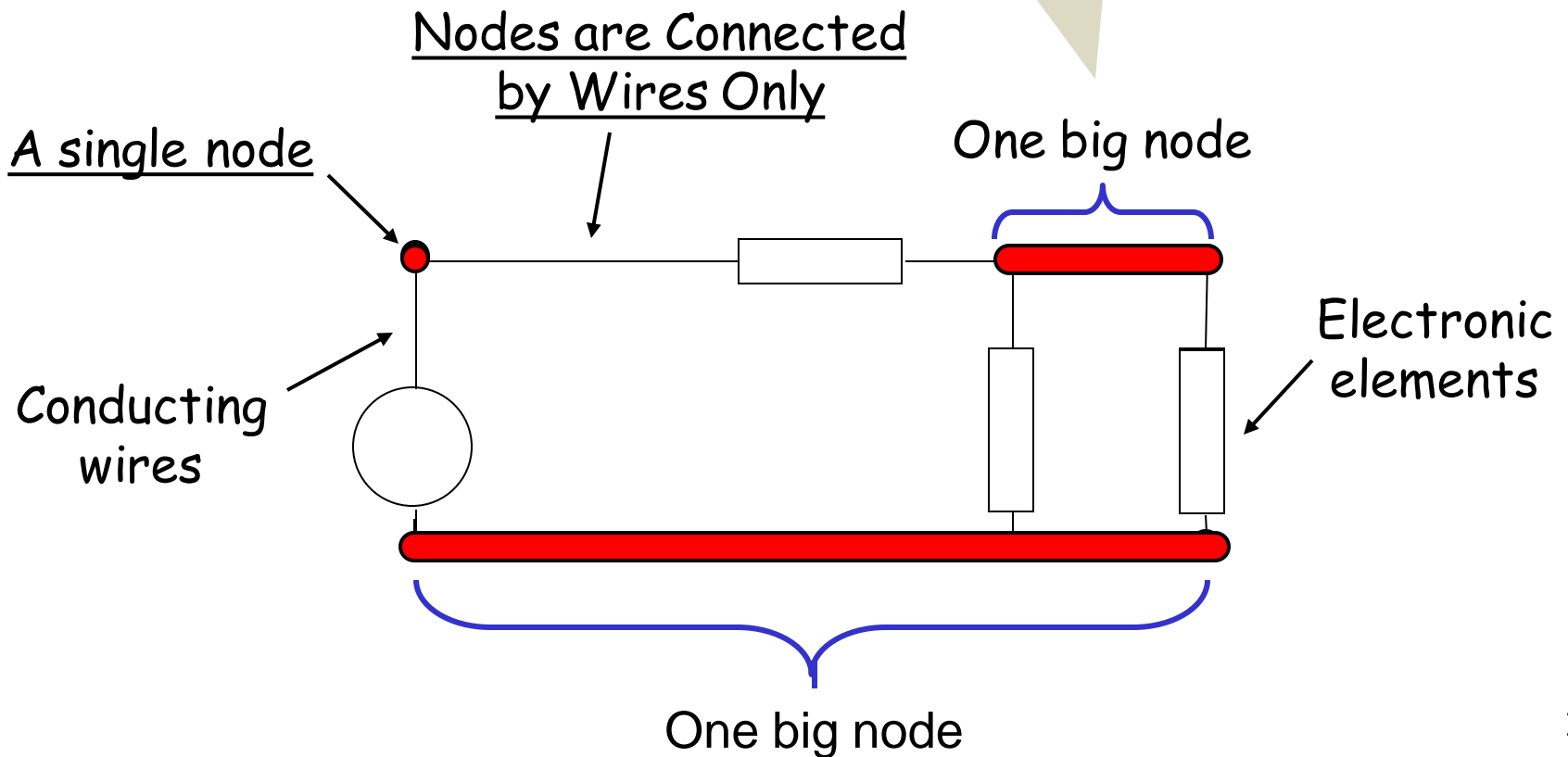
# Electric Circuit

Two or more nodes connected just by **wires** can be considered as one single node.



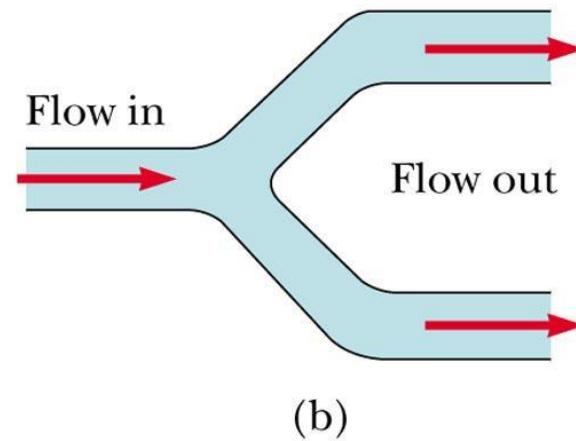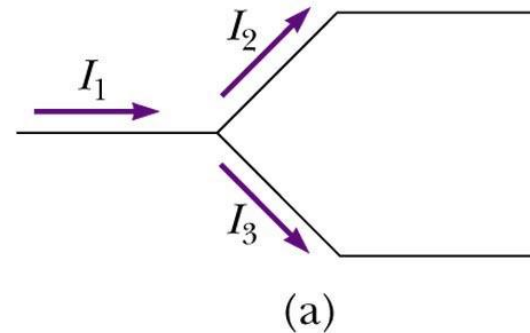
# From Conservation of Charge

- $I_1 = I_2 + I_3$
- Diagram b shows a mechanical analog


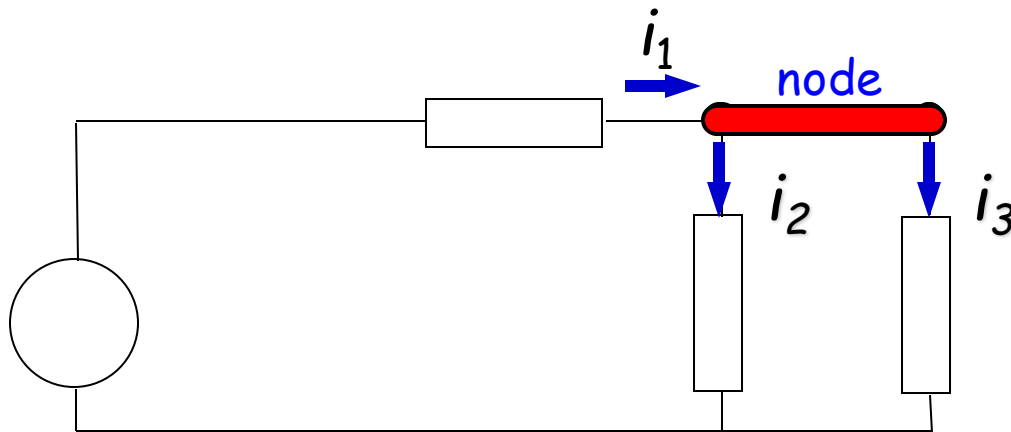
# Kirchhoff's Current Law

- The sum of currents flowing **into** a node must be balanced by the sum of currents flowing **out** of the node.




$i_1$  flows **into** the node

$i_2$  flows **out** of the node

$i_3$  flows **out** of the node

$$i_1 = i_2 + i_3$$

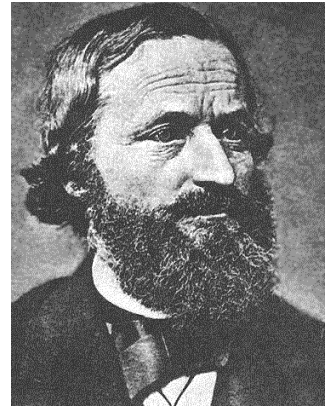


Gustav Kirchhoff  
was an 18th century  
German  
mathematician

# Kirchhoff's Current Law:

$$i_1 = i_2 + i_3$$

- This equation can also be written in the following form:

$$i_1 - i_2 - i_3 = 0$$

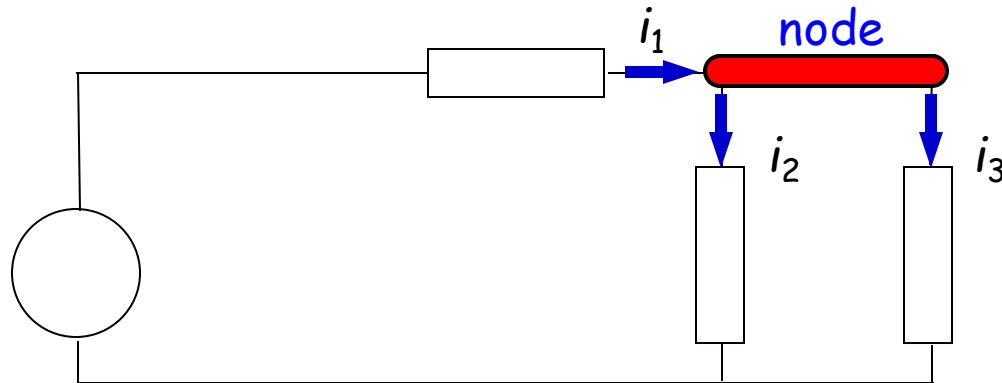

A formal statement of **Kirchhoff's Current Law**:

The sum of *all* the currents **entering** a node is zero.


( $i_2$  and  $i_3$  **leave** the node, hence currents  $-i_2$  and  $-i_3$  **enter** the node.)


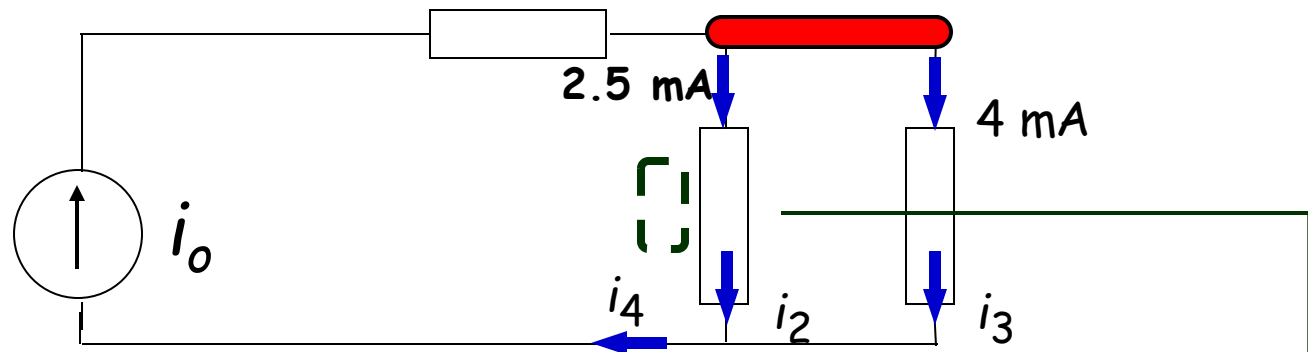
# Example 1: Kirchhoff's Current Law:

Q: How much is the current  $I_o$ ?

A:  $i_o = 2.5 \text{ mA} + 4 \text{ mA} = 6.5 \text{ mA}$




- Note that a "node" need **not** be a **discrete point**
- The dotted circle is a node with 2.5 mA entering
- Hence  $i_2 = 2.5 \text{ mA}$  **exits** the "node".  
Similarly,  $i_3 = 4 \text{ mA}$ .
- From KCL,  $i_4 = i_2 + i_3 = 6.5 \text{ mA}$ , and  $I_o = i_4$
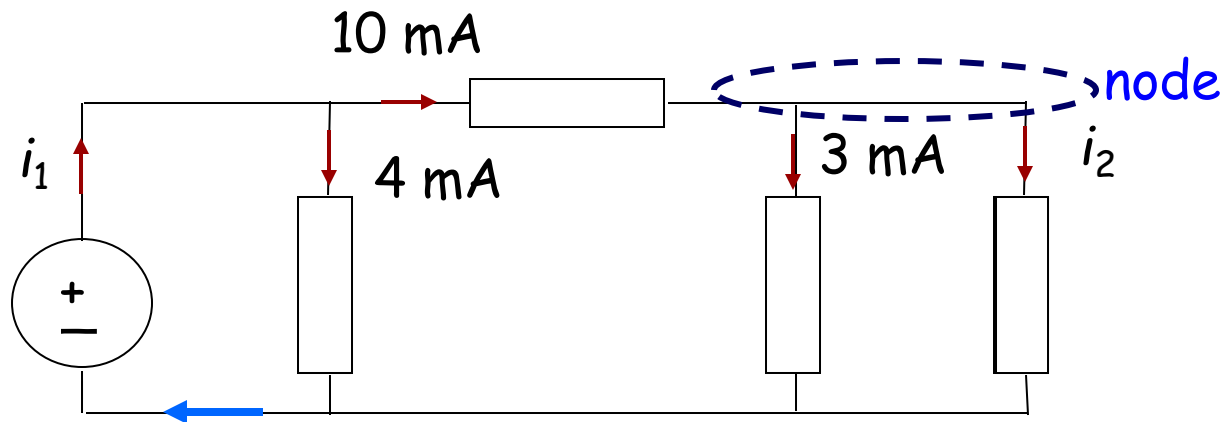
## Example 2: Kirchhoff's Current Law:

Q: How much are the currents  $i_1$  and  $i_2$ ?

A:  $i_2 = 10 \text{ mA} - 3 \text{ mA} = 7 \text{ mA}$   
 $i_1 = 10 \text{ mA} + 4 \text{ mA} = 14 \text{ mA}$



$$4 \text{ mA} + 3 \text{ mA} + 7 \text{ mA} = 14 \text{ mA}$$

Sometimes Kirchhoff's Current Law is abbreviated just by

**KCL**


**Review:** Different ways to state KCL:

- ✓ The sum of *all* currents **entering** a node must be zero.
- ✓ The net current entering a node must be zero.
- ✓ Whatever flows into a node must come out.

more to follow...
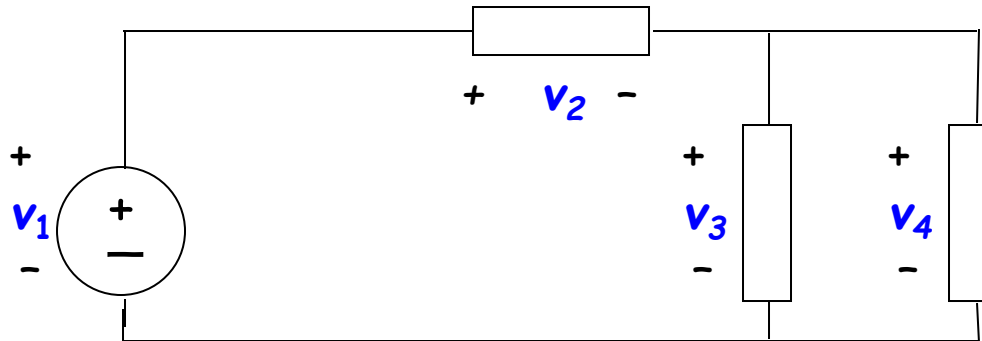
# Voltage (Difference in energy level )


- **Voltages** are measured across the nodes of a network.
- The **direction** of a voltage is indicated by + and - signs.



Remember: The **voltage sources** in the network flow of current through the branches.
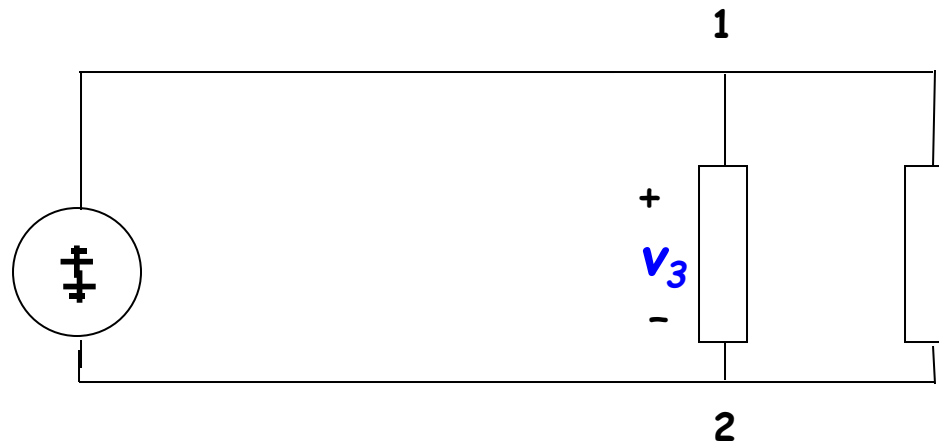
# Every Voltage has a Value and a Polarity

- The polarity is defined by the person drawing the network.
- The value is determined by the properties of the circuit.



## Example:


The plus and minus signs above define the polarity of  $v_3$  as “positive” from node 1 to node 2. Suppose that +5 V appears physically from node 1 to node 2 . Then  $v_3 = 5$  V.

## Converse:

Suppose that +5 V appears physically from node 2 to node 1 . Then  $v_3 = -5$  V.
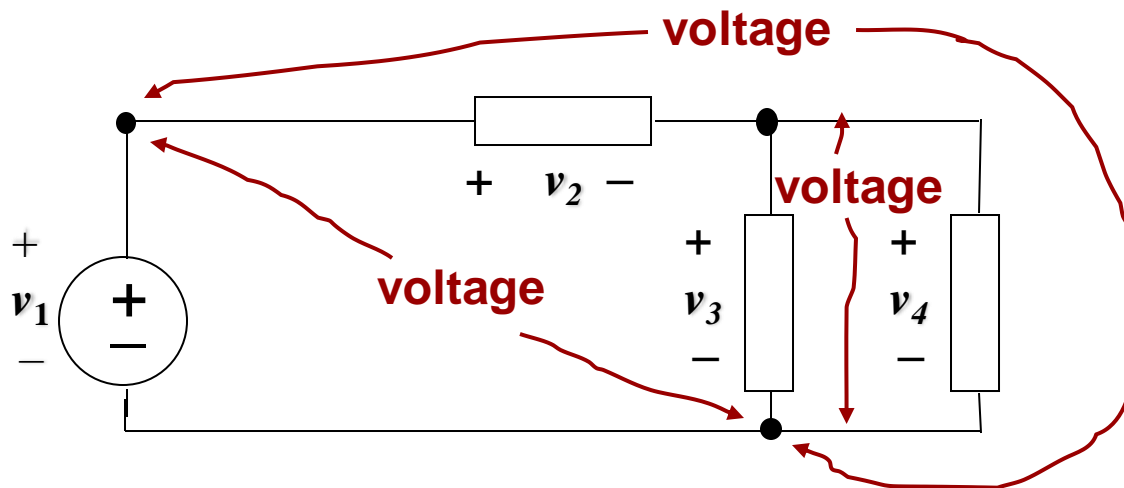
# Kirchhoff's Voltage Law

The voltage measured between any two nodes **does not depend** of the path taken.



Example of KVL:

$$v_1 = v_2 + v_3$$

Similarly:

$$v_1 = v_2 + v_4$$

and:


$$v_3 = v_4$$

# Kirchhoff's Voltage Law:

$$v_1 = v_2 + v_3$$

- This equation can also be written in the following form:

$$-v_1 + v_2 + v_3 = 0$$

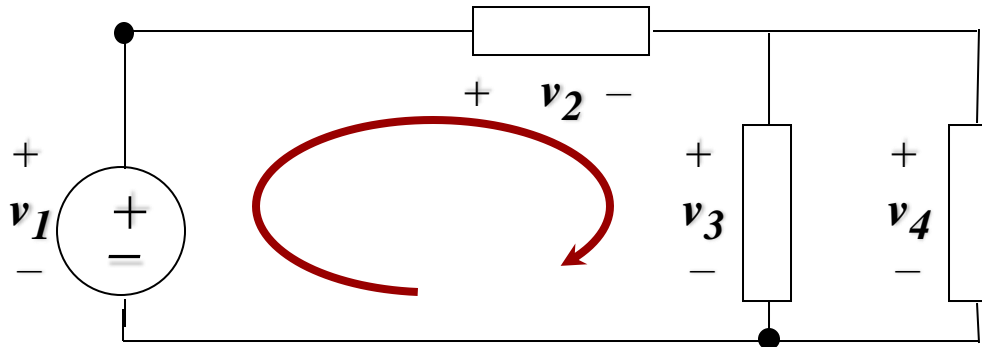


A formal statement of **Kirchhoff's Voltage Law**:

The sum of voltages around a **closed loop** is zero.
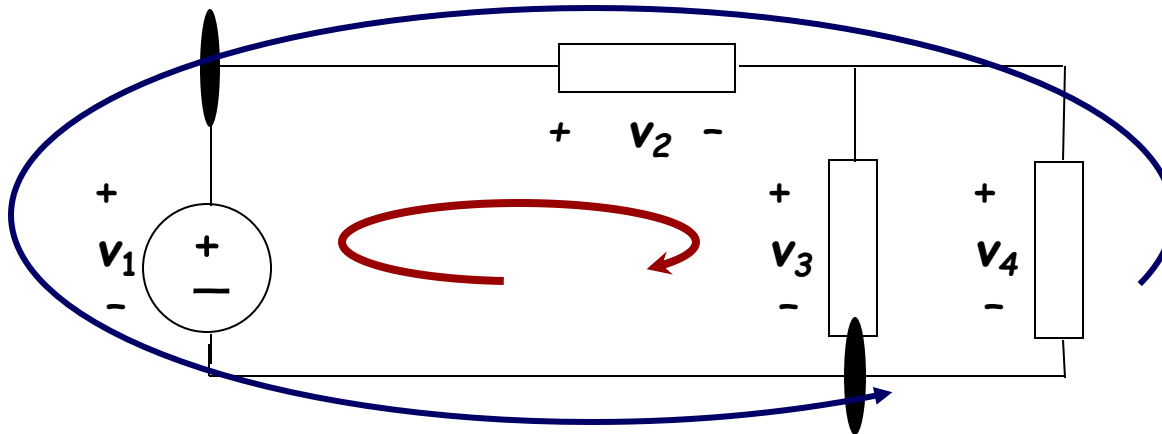
# Using the Formal Definition of KVL

“The sum of voltages around a closed loop is zero.”

- Define an arrow direction around a closed loop.
- Sum the voltages that are encountered around the loop.
- If the arrow first encounters a **plus** sign, enter that voltage with a (+) into the KVL equation.
- If the arrow first encounters a **minus** sign, enter that voltage with a (-) into the KVL equation.



For the inner loop:  $-v_1 + v_2 + v_3 = 0$


For the outer loop:  $-v_4 - v_2 + v_1 = 0$


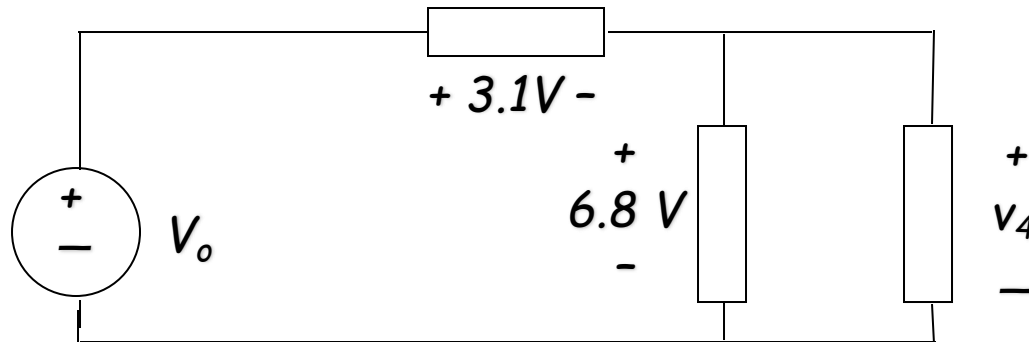
# Example 1: Kirchhoff's Voltage Law:

Q: How much is the voltage  $V_o$ ?

A:  $V_o = 3.1 \text{ V} + 6.8 \text{ V}$



Q: How much is the voltage  $v_4$ ?

A:  $v_4 = 6.8 \text{ V}$


## Example 2: Kirchhoff's Voltage Law:

**Q:** If  $v_1 = 10 \text{ V}$  and  $v_5 = 2 \text{ V}$ , what are  $v_2$ ,  $v_3$ , and  $v_4$ ?

**A:**  $-v_1 + v_2 = 0 \Rightarrow v_2 = -10 \text{ V}$

$-v_2 + v_3 + v_5 = 0 \Rightarrow v_3 = 10 \text{ V} - 2 \text{ V} = 8 \text{ V}$

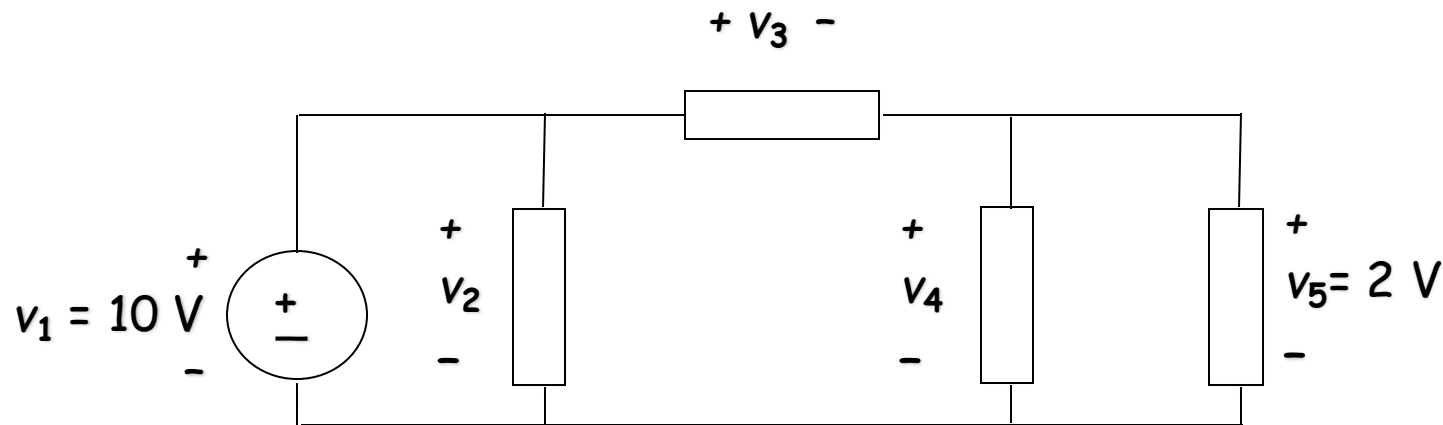$-v_4 + v_5 = 0 \Rightarrow v_4 = 2 \text{ V}$







# Electronic Circuits

Circuits are obtained by connecting electronic elements

Typical electronic elements are

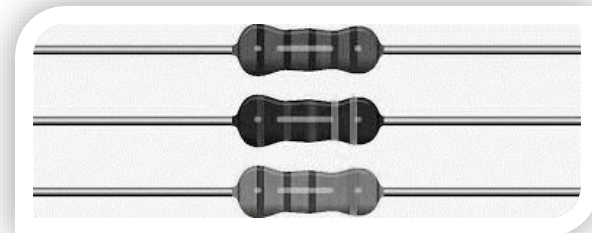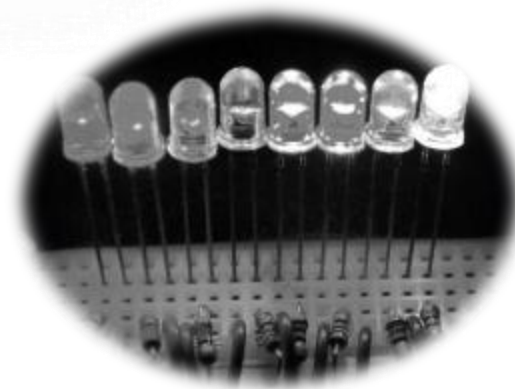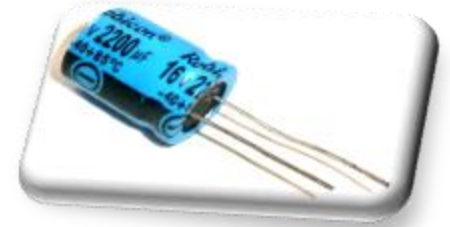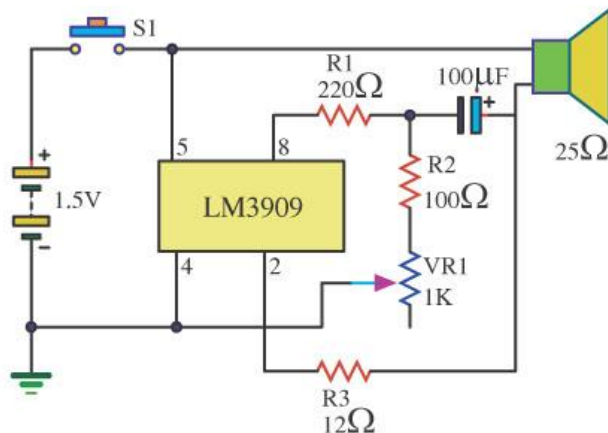- diodes
- resistors,
- capacitors,
- inductors




# Ohm's Law & Resistors



Georg Ohm

Let us remind the Ohm's Law

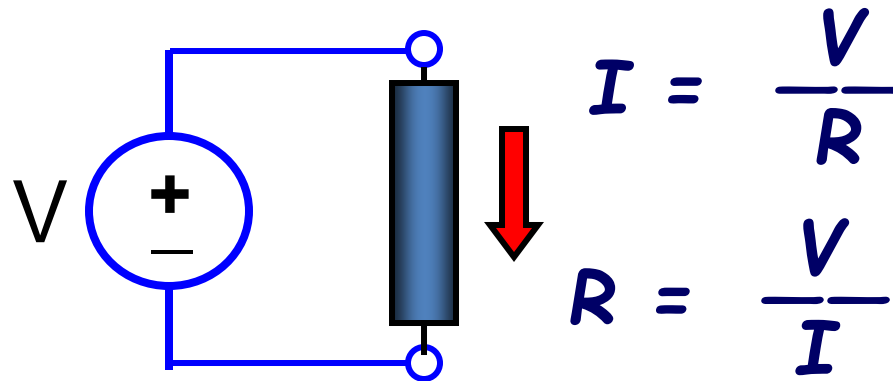


- Assume that the wires are "perfect conductors"
- The unknown circuit element limits the flow of current.
- The resistive element has **resistance**  $R$

# Ohm's Law

Voltage drop across a resistor is proportional to the current flowing through the resistor

$$V = iR$$

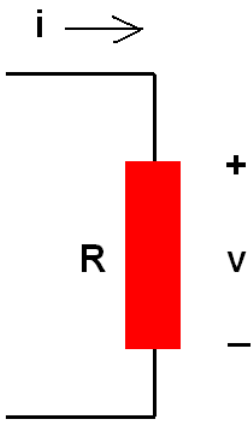


If the resistor is a perfect conductor (or a short circuit)

$R = 0$  ohm, then

$$v = iR = 0 \text{ V}$$

no matter how much current is flowing through the resistor

# Resistors in Series

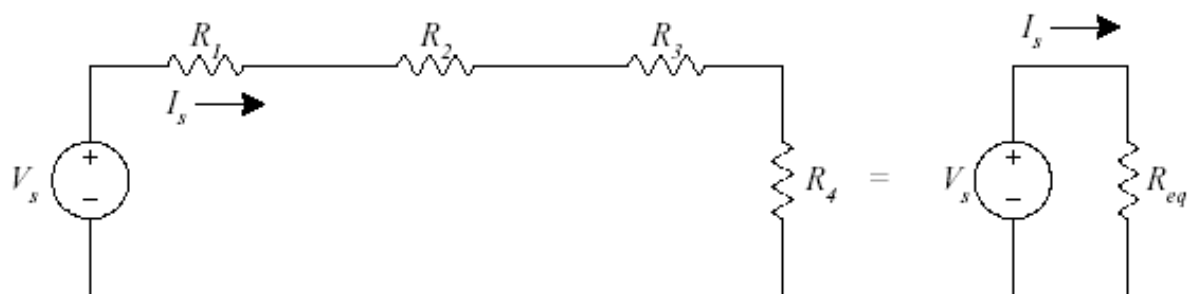


By KVL

$$\begin{aligned} V_s &= R_1 I_s + R_2 I_s + R_3 I_s + R_4 I_s \\ &= I_s (R_1 + R_2 + R_3 + R_4) \\ &= R_{eq} I_s \\ R_{eq} &= R_1 + R_2 + R_2 + R_4 \end{aligned}$$

- Resistors in series add

# Resistors in Parallel

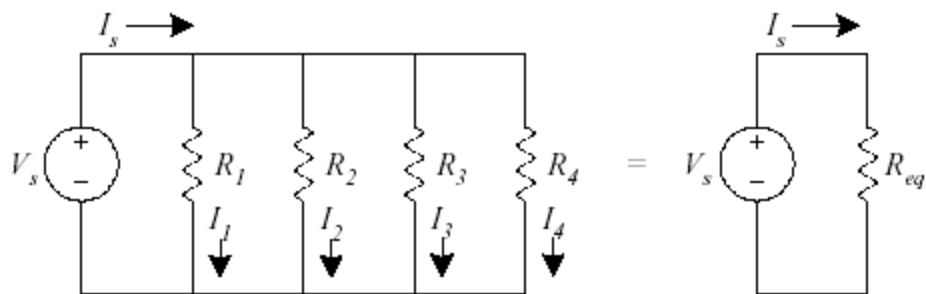


$$\begin{aligned} I_s &= I_1 + I_2 + I_3 + I_4 \\ &= V_s/R_1 + V_s/R_2 + V_s/R_3 + V_s/R_4 \\ &= V_s \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) \\ &= \frac{V_s}{R_{eq}} \end{aligned}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$$

# Resistors in Parallel

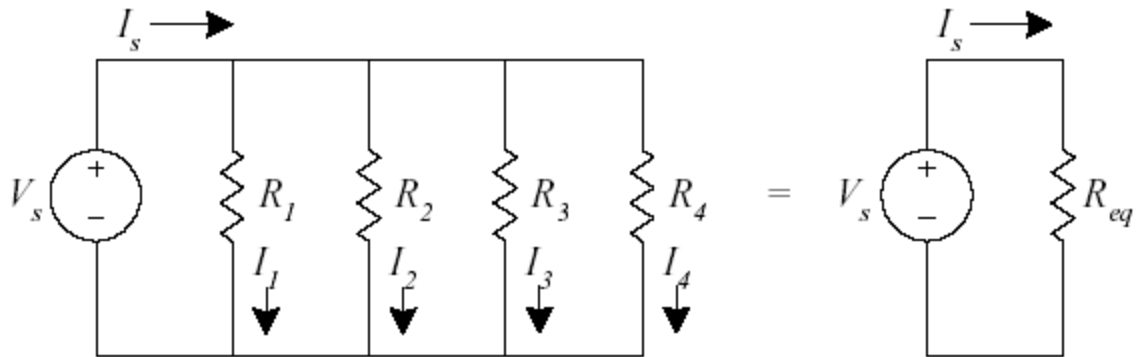


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$
$$G_{eq} = G_1 + G_2 + G_3 + G_4$$

- Resistors in parallel have a more complicated relationship
- Easier to express in terms of conductance
- For two resistors:  $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$



# Voltage Divider

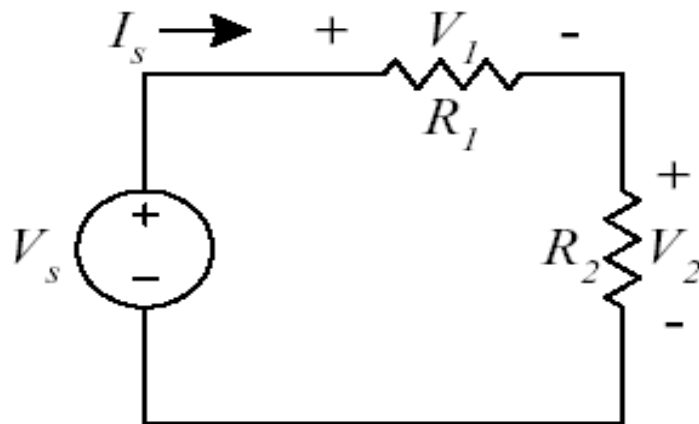

$$R_{eq} = R_1 + R_2$$

$$I_s = \frac{V_s}{R_{eq}}$$

$$= \frac{V_s}{R_1 + R_2}$$


$$V_2 = I_s R_2$$

$$= V_s \frac{R_2}{R_1 + R_2}$$

$$V_1 = I_s R_1$$


$$= V_s \frac{R_1}{R_1 + R_2}$$
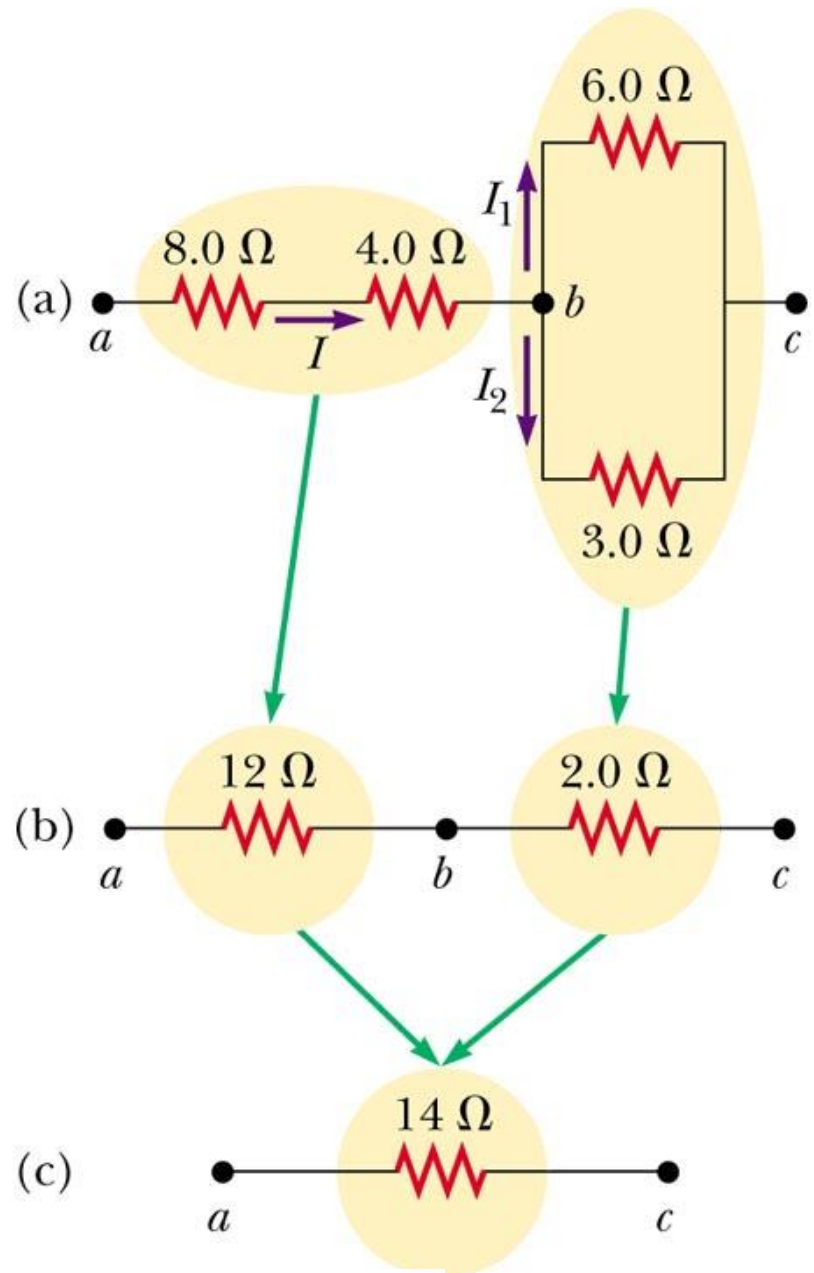
# Equivalent Resistance - Complex Circuit


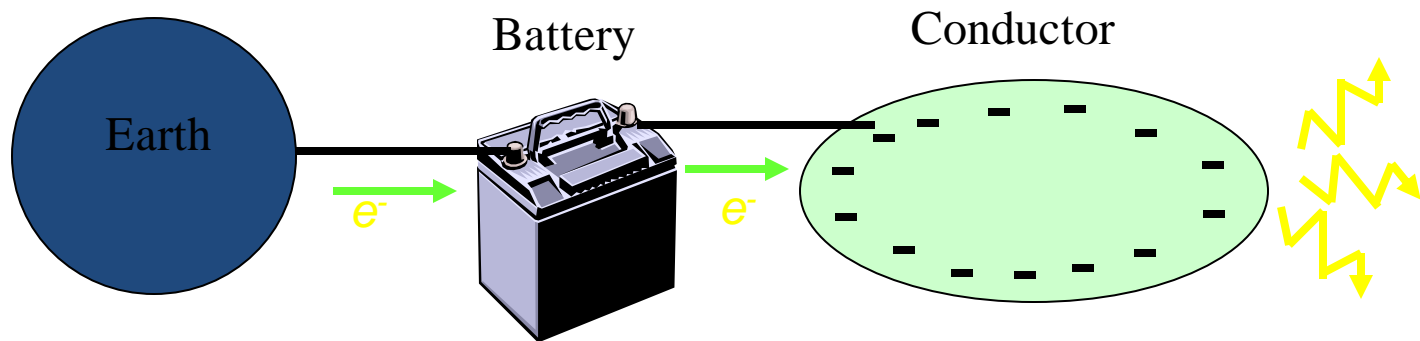
# Maximum Charge on a Conductor


A battery establishes a difference of potential that can pump electrons  $e^-$  from a ground (earth) to a conductor



There is a limit to the amount of charge that a conductor can hold without leaking to the air. There is a certain capacity for holding charge.
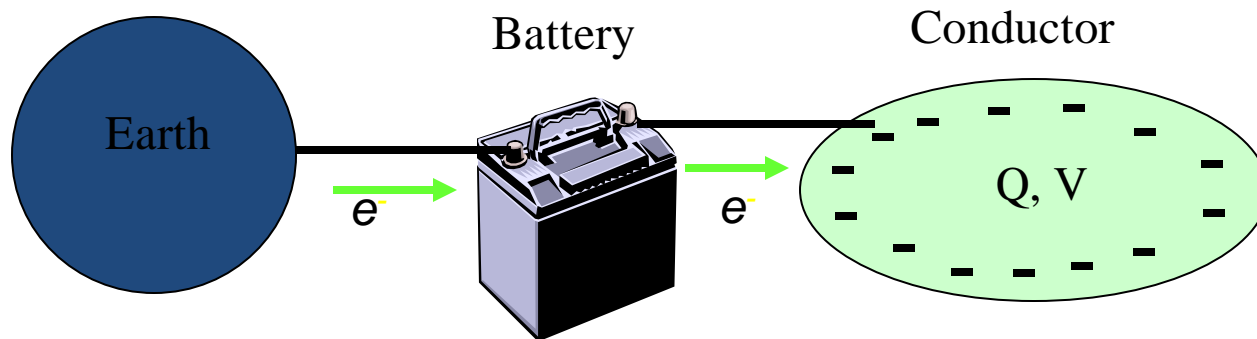
# Capacitance

The capacitance  $C$  of a conductor is defined as the ratio of the charge  $Q$  on the conductor to the potential  $V$  produced.




**Capacitance:**

$$C = \frac{Q}{V}; \quad \text{Units: Coulombs per volt}$$
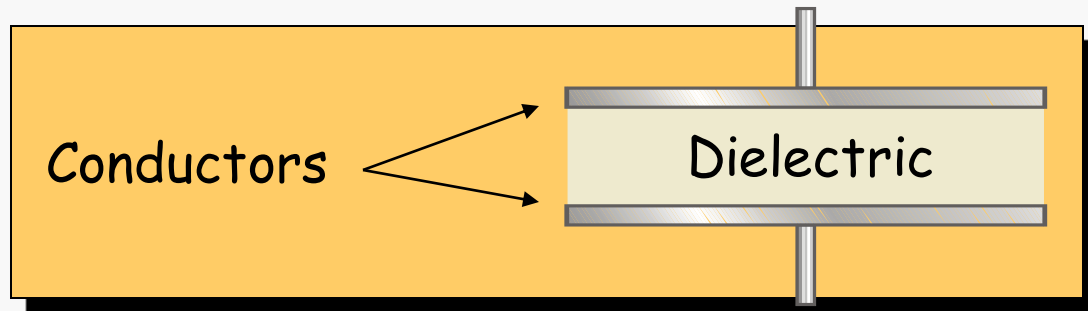
# The Capacitor

**Capacitors** are one of the fundamental passive components. In its most basic form, it is composed of two plates separated by a dielectric.

The ability to store charge is the definition of **capacitance**.




$$C = \frac{Q}{V}; \quad \text{Units : Coulombs per volt}$$

# The Capacitor

The charging process...

Steadily charged

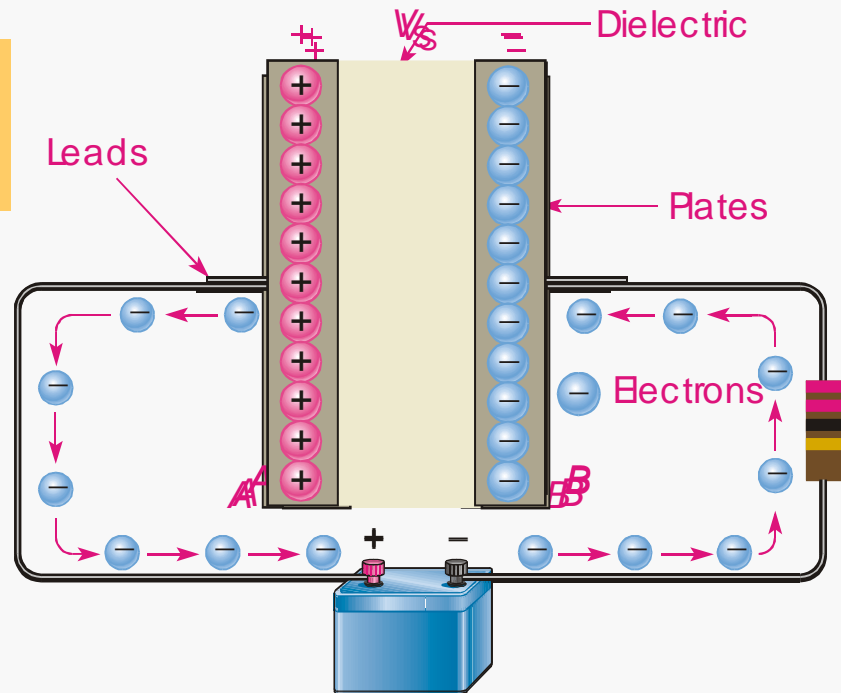

A capacitor with stored charge can act as a temporary battery.


# Capacitors in Parallel:

$$q_1 = C_1 V, \quad q_2 = C_2 V, \quad \text{and} \quad q_3 = C_3 V.$$


$$q = q_1 + q_2 + q_3 = (C_1 + C_2 + C_3)V.$$

$$C_{\text{eq}} = \frac{q}{V} = C_1 + C_2 + C_3,$$
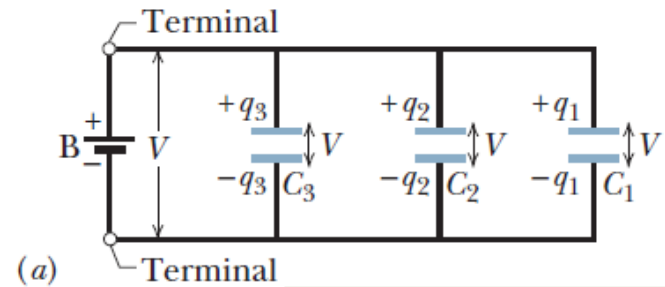
$$C_{\text{eq}} = \sum_{j=1}^n C_j \quad (n \text{ capacitors in parallel}).$$



Parallel capacitors and their equivalent have the same  $V$  ("par- $V$ ").

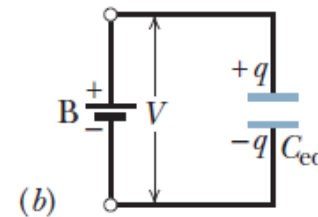

**Fig. 25-8** (a) Three capacitors connected in parallel to battery B. The battery maintains potential difference  $V$  across its terminals and thus across *each* capacitor. (b) The equivalent capacitor, with capacitance  $C_{\text{eq}}$ , replaces the parallel combination.

# Capacitors in Series:


$$V_1 = \frac{q}{C_1}, \quad V_2 = \frac{q}{C_2}, \quad \text{and} \quad V_3 = \frac{q}{C_3}.$$

$$V = V_1 + V_2 + V_3 = q \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right).$$


$$C_{\text{eq}} = \frac{q}{V} = \frac{1}{1/C_1 + 1/C_2 + 1/C_3},$$

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}.$$
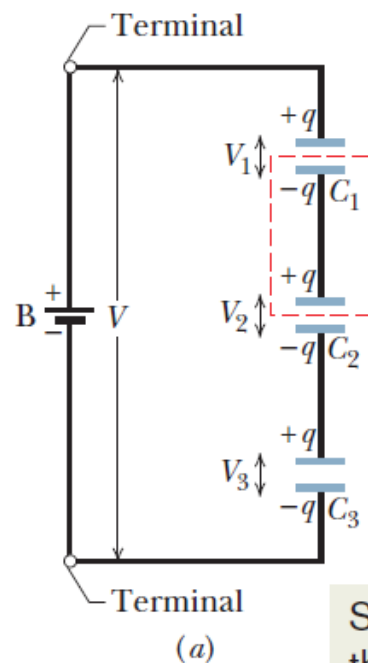
$$\frac{1}{C_{\text{eq}}} = \sum_{j=1}^n \frac{1}{C_j} \quad (n \text{ capacitors in series}).$$



Series capacitors and their equivalent have the same  $q$  ("seri- $q$ ").

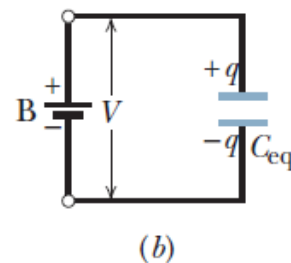


**Fig. 25-9** (a) Three capacitors connected in series to battery B. The battery maintains potential difference  $V$  between the top and bottom plates of the series combination. (b) The equivalent capacitor, with capacitance  $C_{\text{eq}}$ , replaces the series combination.

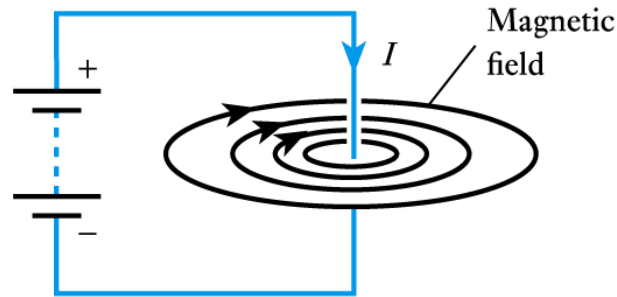


# Electromagnetism


A wire carrying a current  $I$  produces a magnetic field



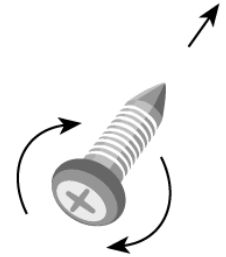
(a) The magnetic field about a current-carrying wire



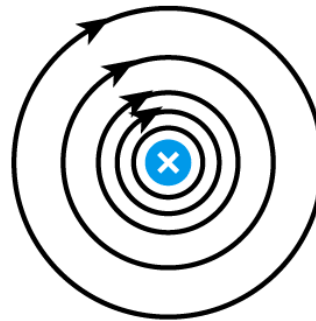(b) The direction of rotation and motion of a woodscrew



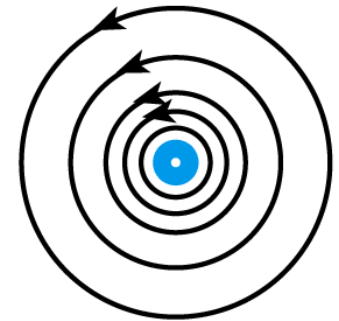(c) The magnetic field about a current flowing into the page




(d) The magnetic field about a current flowing out of the page

# Inductance
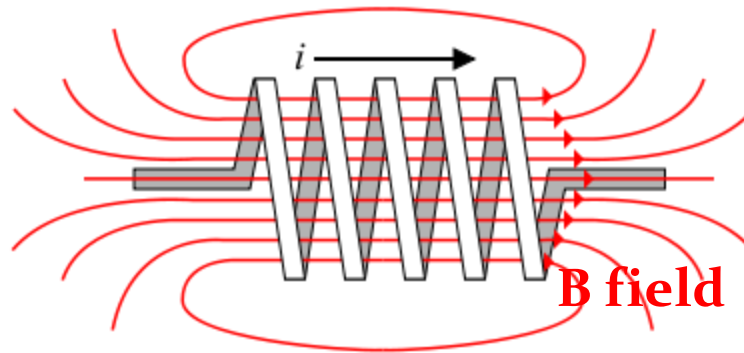
## Energy Storage Devices

Stores energy in an magnetic field created by the electric current flowing through it.

- The flow of current through an inductor creates a magnetic field



- If the current flowing through the inductor drops, the magnetic field will also decrease and energy is released through the generation of a current.




# Inductors

- Generally - coil of conducting wire
  - Usually wrapped around a solid core. If no core is used, then the inductor is said to have an 'air core'.



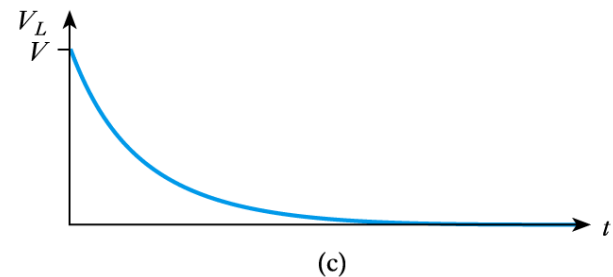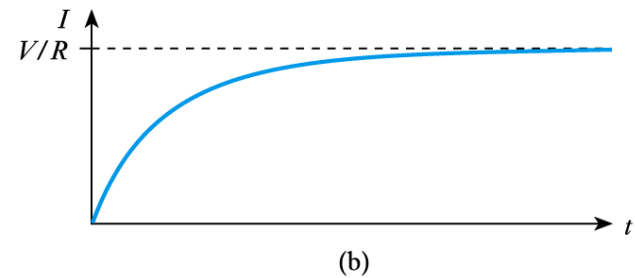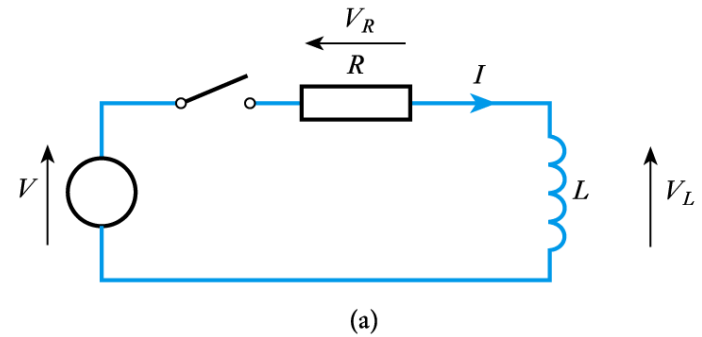
# Voltage and Current Relation


- Consider the circuit shown here
  - inductor is initially un-energised
    - current through it will be zero
  - switch is closed at  $t = 0$
  - $I$  is initially zero
    - hence  $V_R$  is initially 0
    - hence  $V_L$  is initially  $V$
  - as the inductor is energised:
    - $I$  increases
    - $V_R$  increases
    - hence  $V_L$  decreases
    - we have exponential behaviour



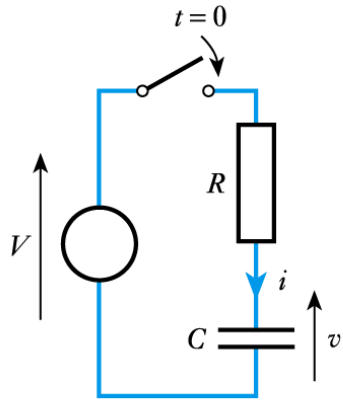
# Both the voltage and current have an exponential forms



(a)

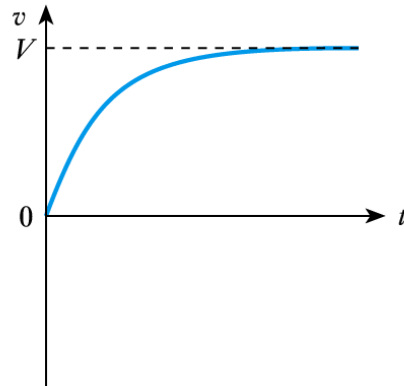

(b)

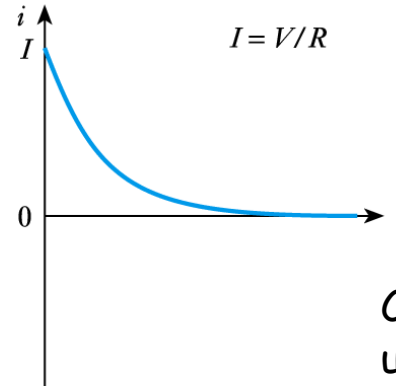


(c)


$$i_c = C \frac{dv}{dt}$$

$C$ , capacitance, has the units of Farad (F)


$$1 \text{ F} = 1 \text{ A.s/V}$$

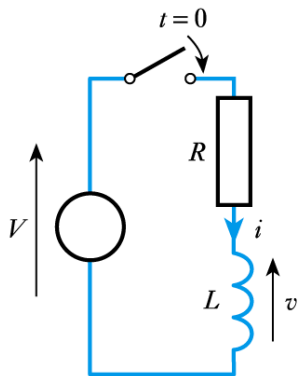

(a)

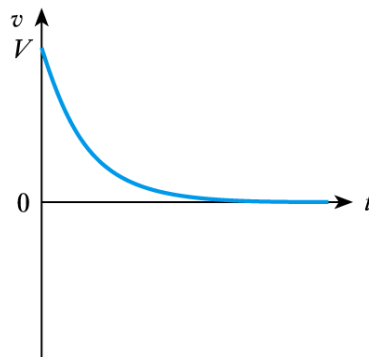

(b)

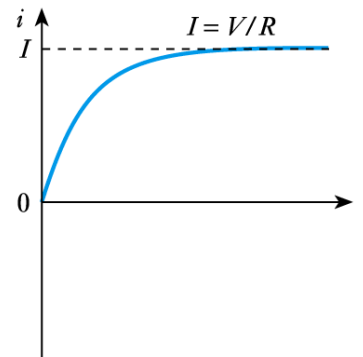


(c)

$$v_L = L \frac{di}{dt}$$

$L$ , inductance, has the units of Henries (H)

$$1 \text{ H} = 1 \text{ V.s/A}$$

# Inductors in Series

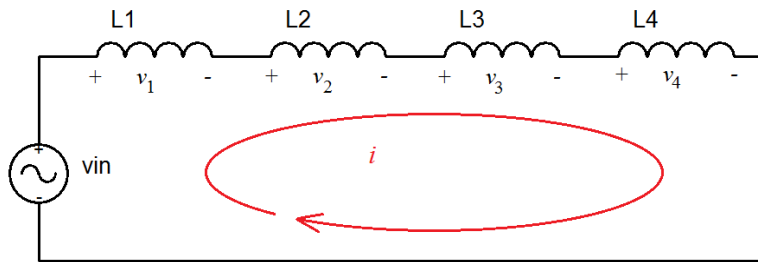

$$v_{in} = v_1 + v_2 + v_3 + v_4$$

$$v_1 = L_1 \frac{di}{dt} \qquad v_2 = L_2 \frac{di}{dt}$$


$$v_3 = L_3 \frac{di}{dt} \qquad v_4 = L_4 \frac{di}{dt}$$

$$v_{in} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + L_4 \frac{di}{dt}$$

$$v_{in} = L_{eq} \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 + L_3 + L_4$$

# Inductors in Parallel

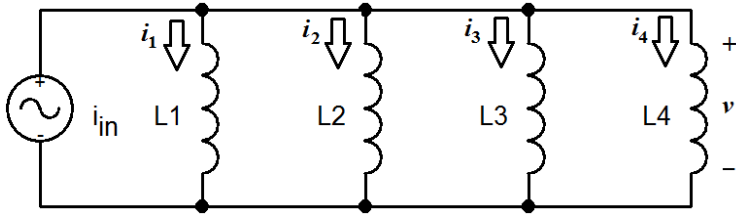

$$i_{in} = i_1 + i_2 + i_3 + i_4$$

$$i_1 = \frac{1}{L_1} \int_{t_0}^{t_1} v dt$$

$$i_2 = \frac{1}{L_2} \int_{t_0}^{t_1} v dt$$

$$i_3 = \frac{1}{L_3} \int_{t_0}^{t_1} v dt$$

$$i_4 = \frac{1}{L_4} \int_{t_0}^{t_1} v dt$$

$$i_{in} = \frac{1}{L_1} \int_{t_0}^{t_1} v dt + \frac{1}{L_2} \int_{t_0}^{t_1} v dt + \frac{1}{L_3} \int_{t_0}^{t_1} v dt + \frac{1}{L_4} \int_{t_0}^{t_1} v dt$$

$$i_{in} = \frac{1}{L_{eq}} \int_{t_0}^{t_1} v dt$$

$$L_{eq} = \left[ \left( \frac{1}{L_1} \right) + \left( \frac{1}{L_2} \right) + \left( \frac{1}{L_3} \right) + \left( \frac{1}{L_4} \right) \right]^{-1}$$


# Example 1

- Determine  $I$ , the current flowing out of the voltage source.
  - Use KCL
    - $1.9 \text{ mA} + 0.5 \text{ mA} + I$  are entering the node.
    - $3 \text{ mA}$  is leaving the node.
  - $V1$  is generating power.

$$1.9 \text{ mA} + 0.5 \text{ mA} + I = 3 \text{ mA}$$

$$I = 3 \text{ mA} - (1.9 \text{ mA} + 0.5 \text{ mA})$$

$$I = 0.6 \text{ mA}$$

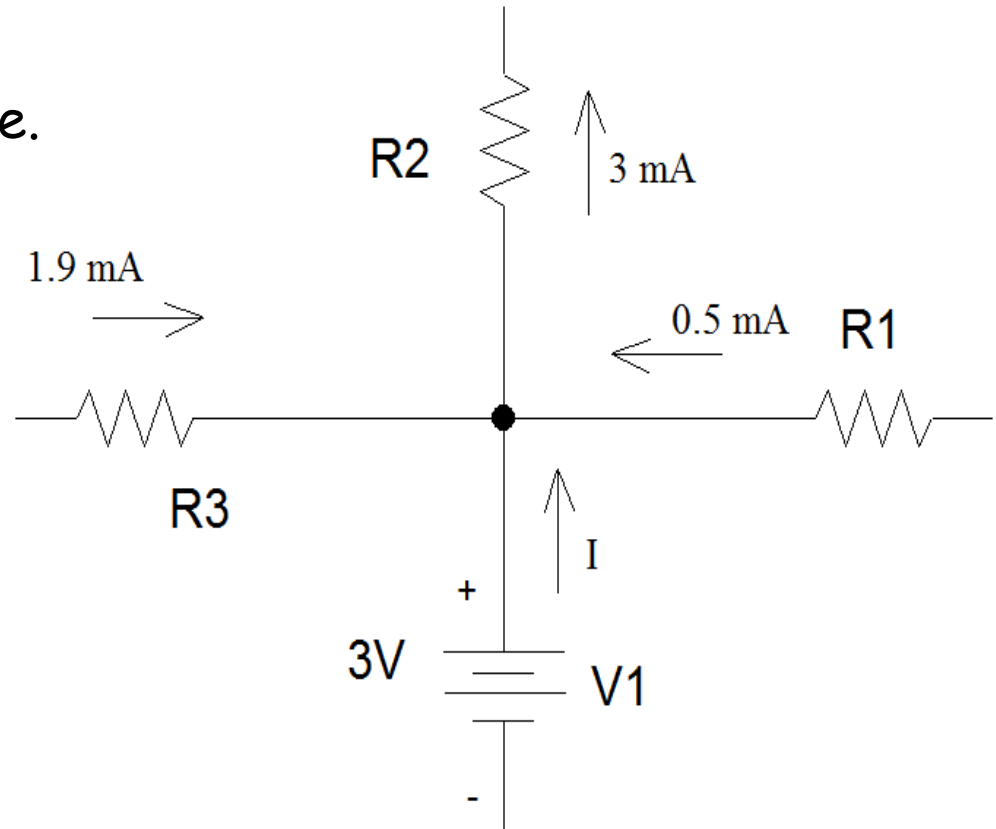




# Example 2

- Suppose the current through R2 was entering the node and the current through R3 was leaving the node.
  - Use KCL
    - $3\text{ mA} + 0.5\text{ mA} + I$  are entering the node.
    - $1.9\text{ mA}$  is leaving the node
  - V1 is dissipating power.

$$3\text{mA} + 0.5\text{mA} + I = 1.9\text{mA}$$


$$I = 1.9\text{mA} - (3\text{mA} + 0.5\text{mA})$$

$$I = -1.6\text{mA}$$

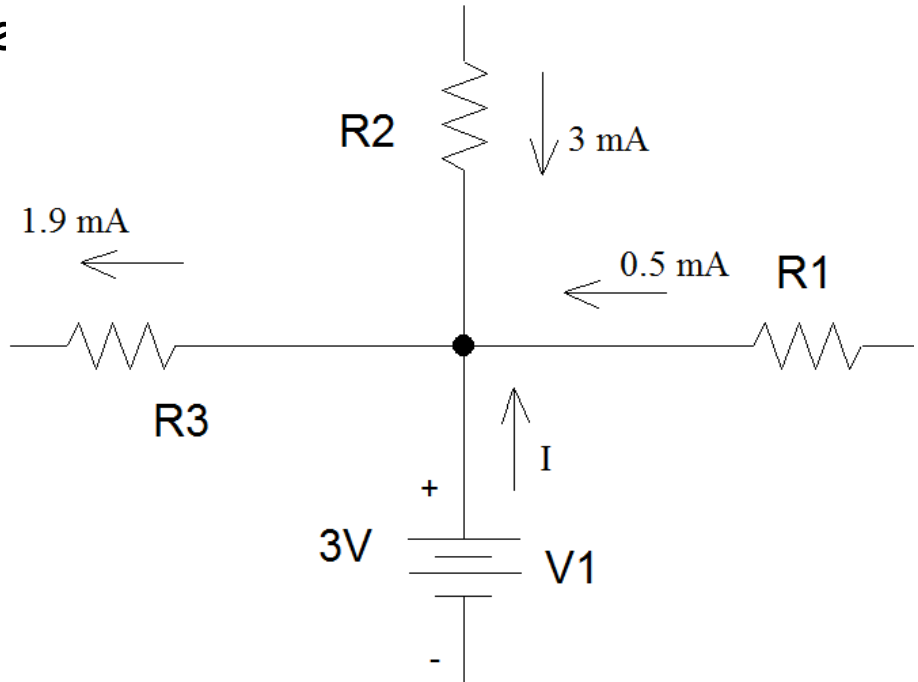

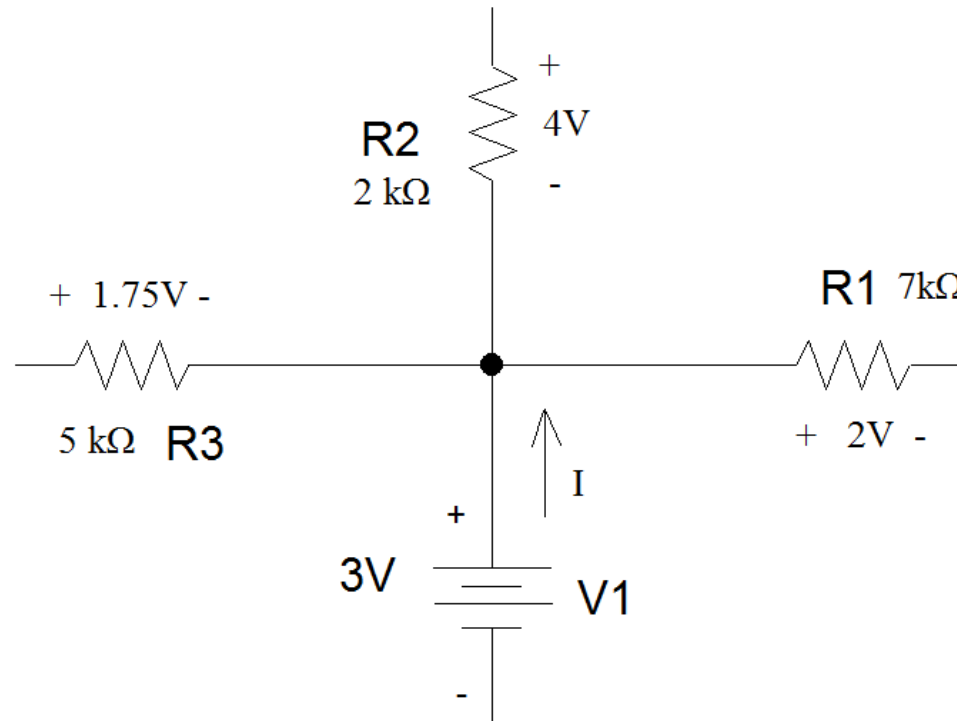
# Example 3

- If voltage drops are given instead of currents, you need to apply Ohm's Law to determine the current flowing through each of the resistors before you can find the current flowing out of the voltage supply.


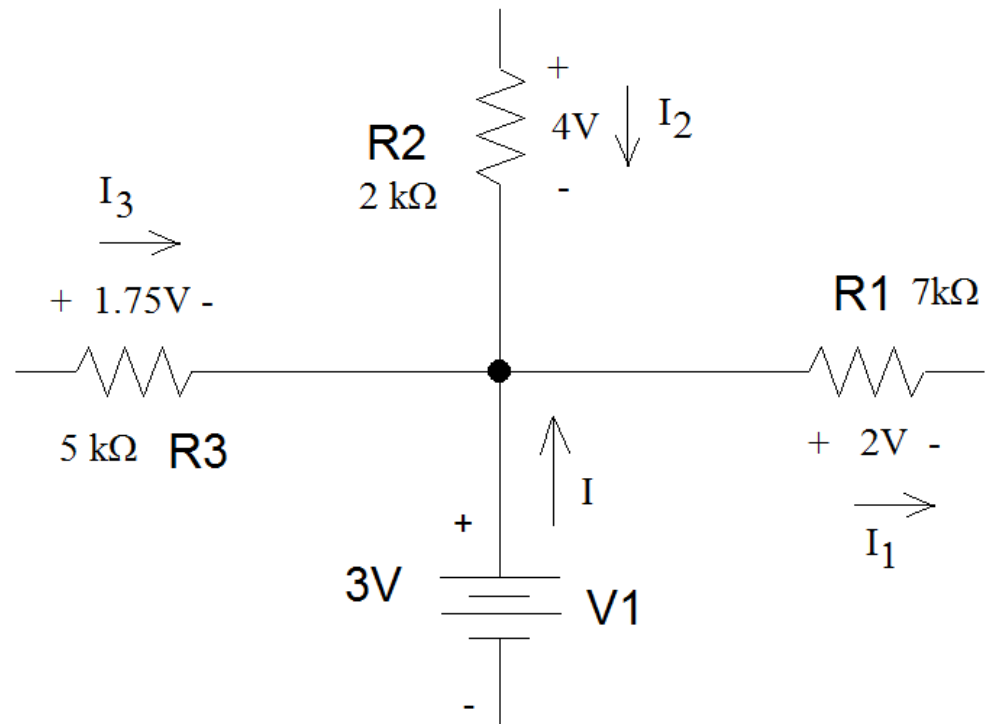
# Example 3 (con't)

- For power dissipating components such as resistors, passive sign convention means that current flows into the resistor at the terminal has the + sign on the voltage drop and leaves out the terminal that has the - sign.




# Example 3 (con't)

$$I_1 = 2V / 7k\Omega = 0.286mA$$


$$I_2 = 4V / 2k\Omega = 2mA$$

$$I_3 = 1.75V / 5k\Omega = 0.35mA$$

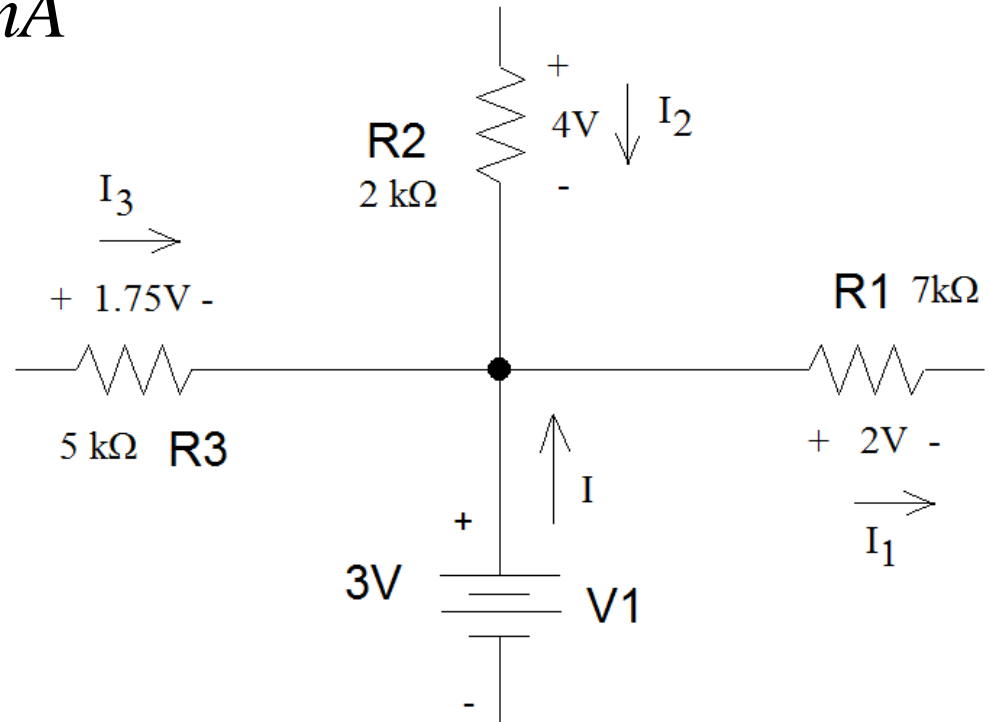
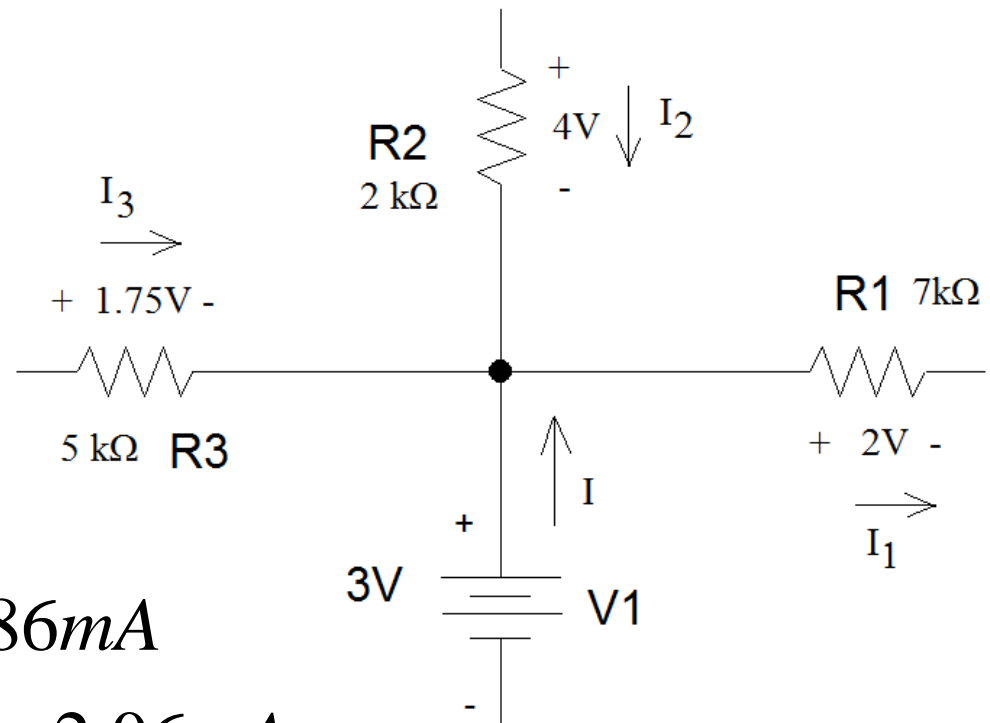
# Example 3 (con't)

- $I_1$  is leaving the node.
- $I_2$  is entering the node.
- $I_3$  is entering the node.
- $I$  is entering the node.




$$I_2 + I_3 + I = I_1$$

$$2mA + 0.35mA + I = 0.286mA$$

$$I = 0.286mA - 2.35mA = -2.06mA$$

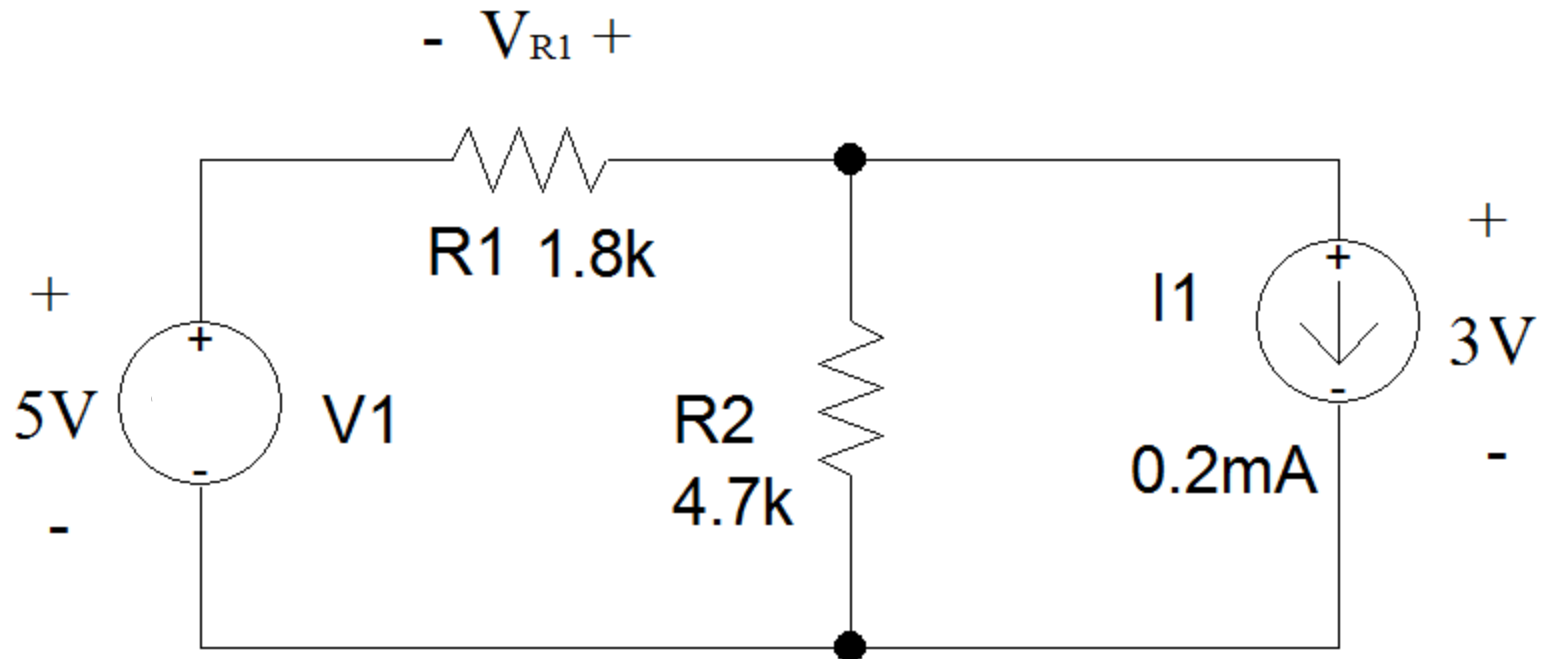
# Example 4

- Find the voltage across  $R1$ . Note that the polarity of the voltage has been assigned in the circuit schematic.
  - First, define a loop that include  $R1$ .



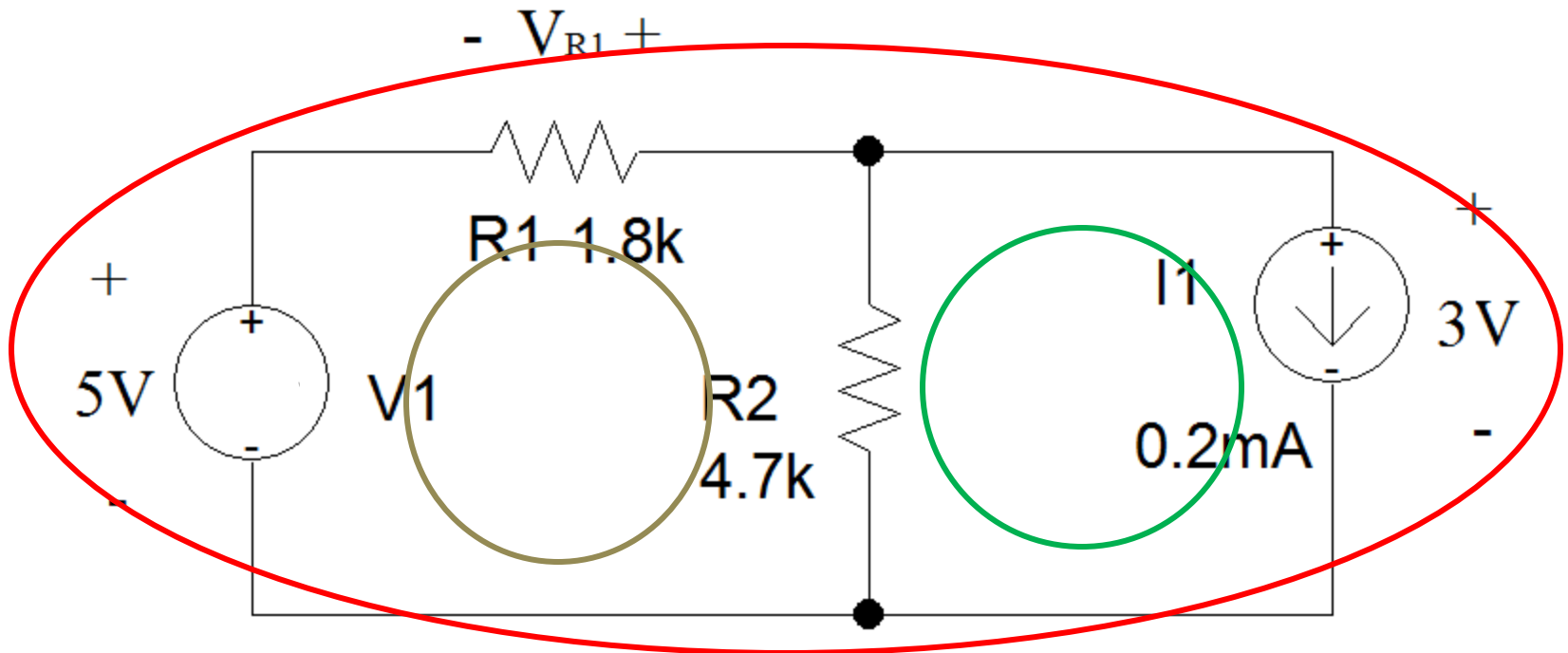
# Example 4 (con't)

- There are three possible loops in this circuit - only two include  $R_1$ .
  - Either loop may be used to determine  $V_{R1}$ .


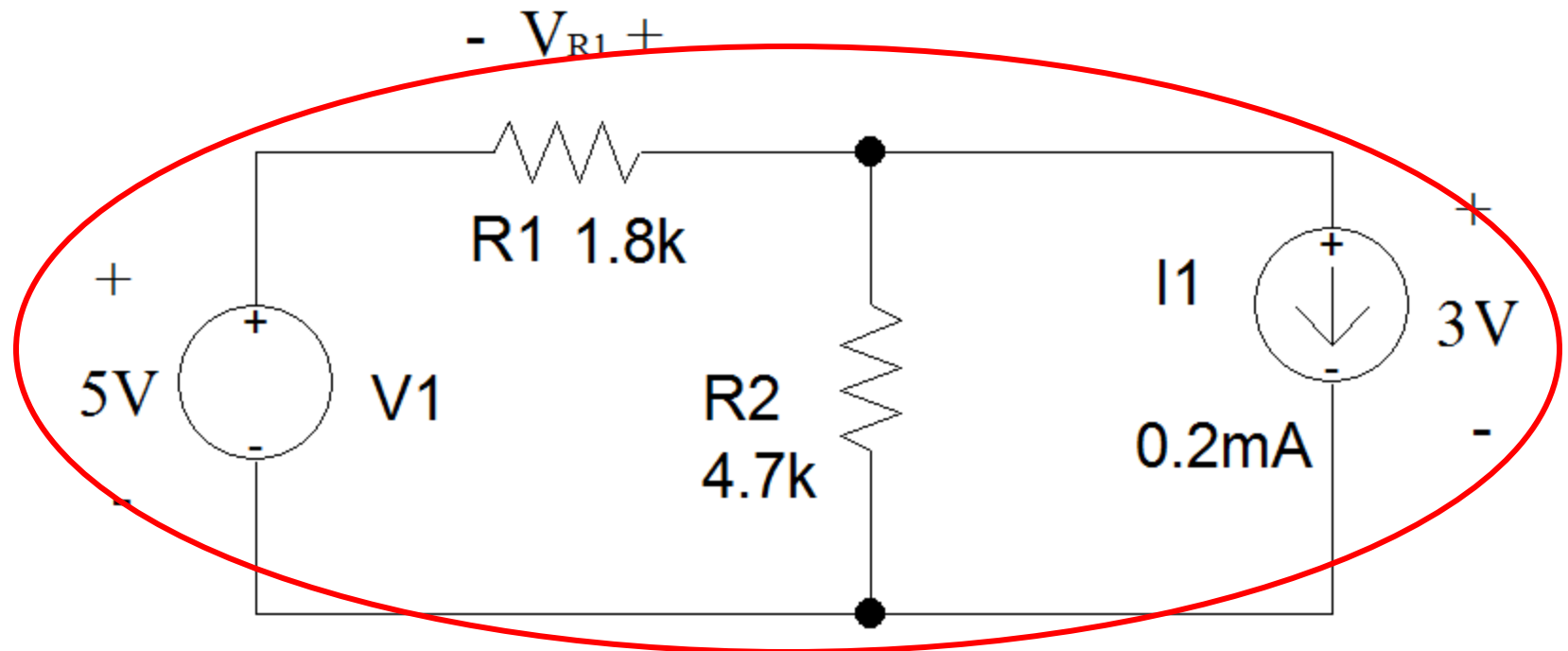
# Example 4 (con't)


- If the outer loop is used:
  - Follow the loop clockwise.




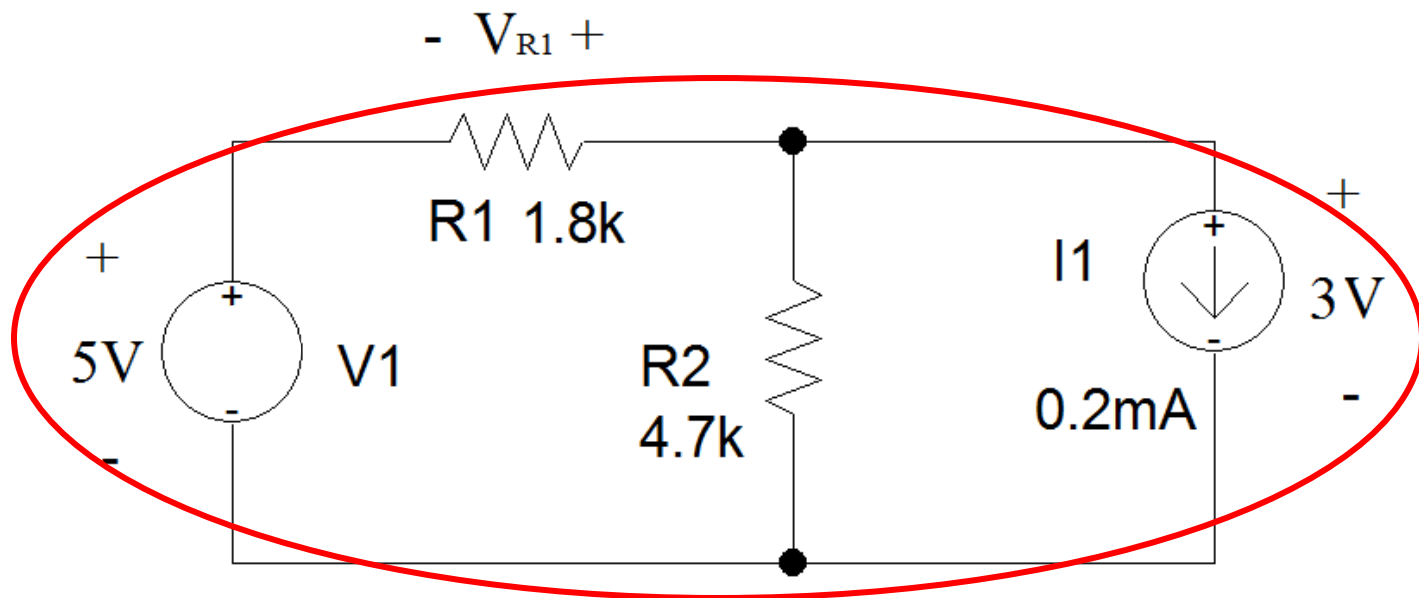
# Example 4 (con't)

- Follow the loop in a clockwise direction.
- The 5V drop across V1 is a voltage rise.
- $V_{R1}$  should be treated as a voltage rise.
- The loop enters on the positive side of the CURRENT source and exits out the negative side. This is a voltage drop as the voltage becomes less positive as you move through the component.




# Example 4 (con't)

By convention, voltage drops are added and voltage rises are subtracted in KVL.


$$-5V - V_{R1} + 3V = 0$$

$$V_{R1} = -2V$$

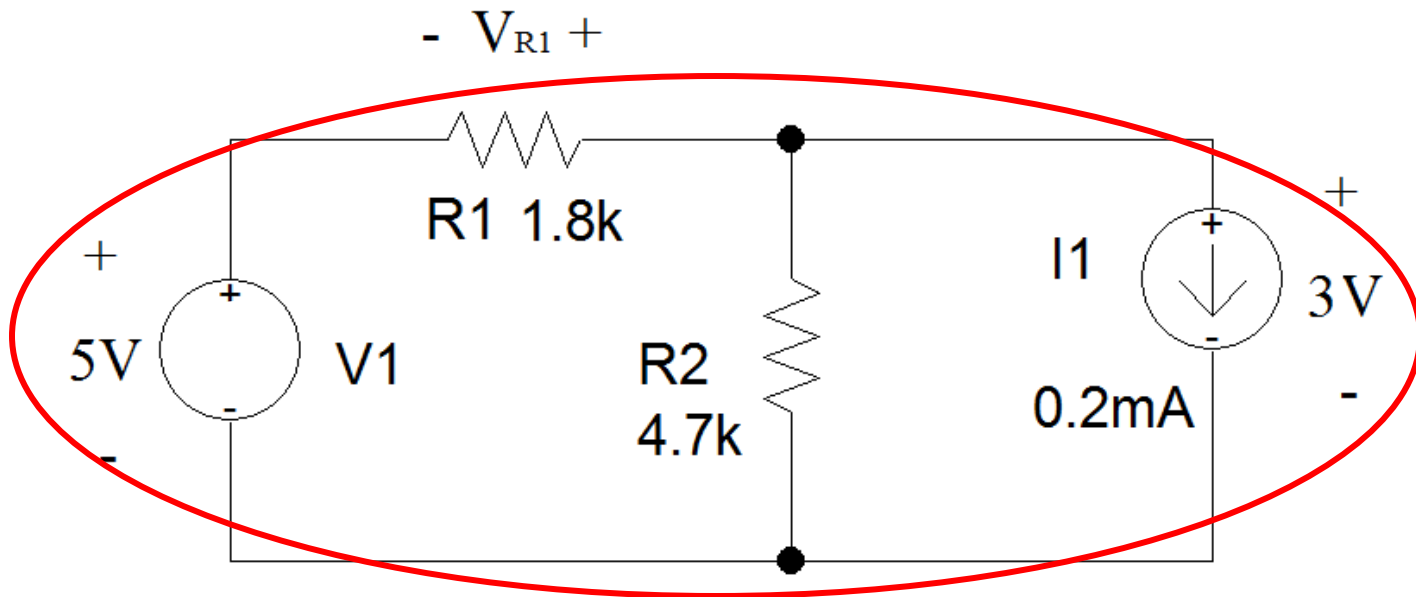
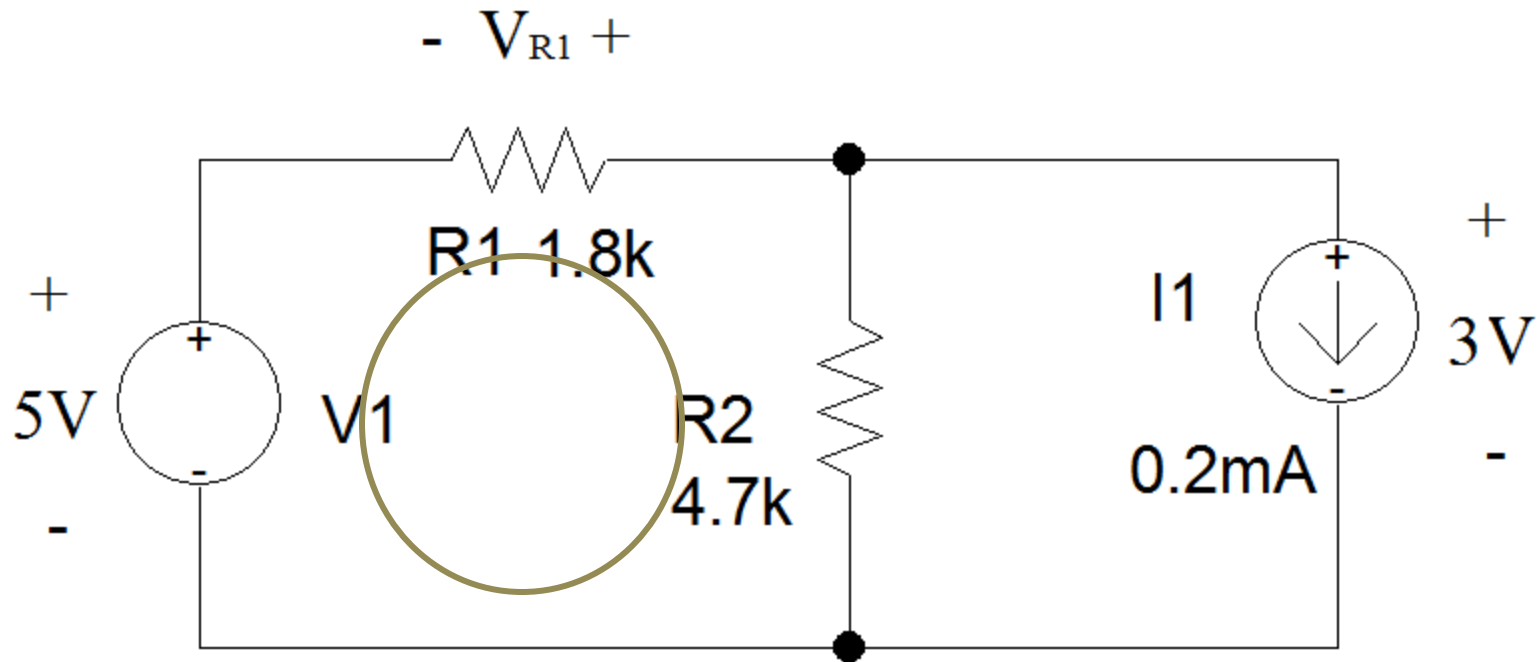
# Example 4 (con't)


- Suppose you chose the green loop instead.
  - Since  $R_2$  is in parallel with  $I_1$ , the voltage drop across  $R_2$  is also 3V.



# Example 4 (con't)

- The 5V drop across V1 is a voltage rise.
- $V_{R1}$  should be treated as a voltage rise.
- The loop enters R2 on the positive side and exits out the negative side. This is a voltage drop as the voltage becomes less positive as you move through the component.

$$- V_{R1} +$$

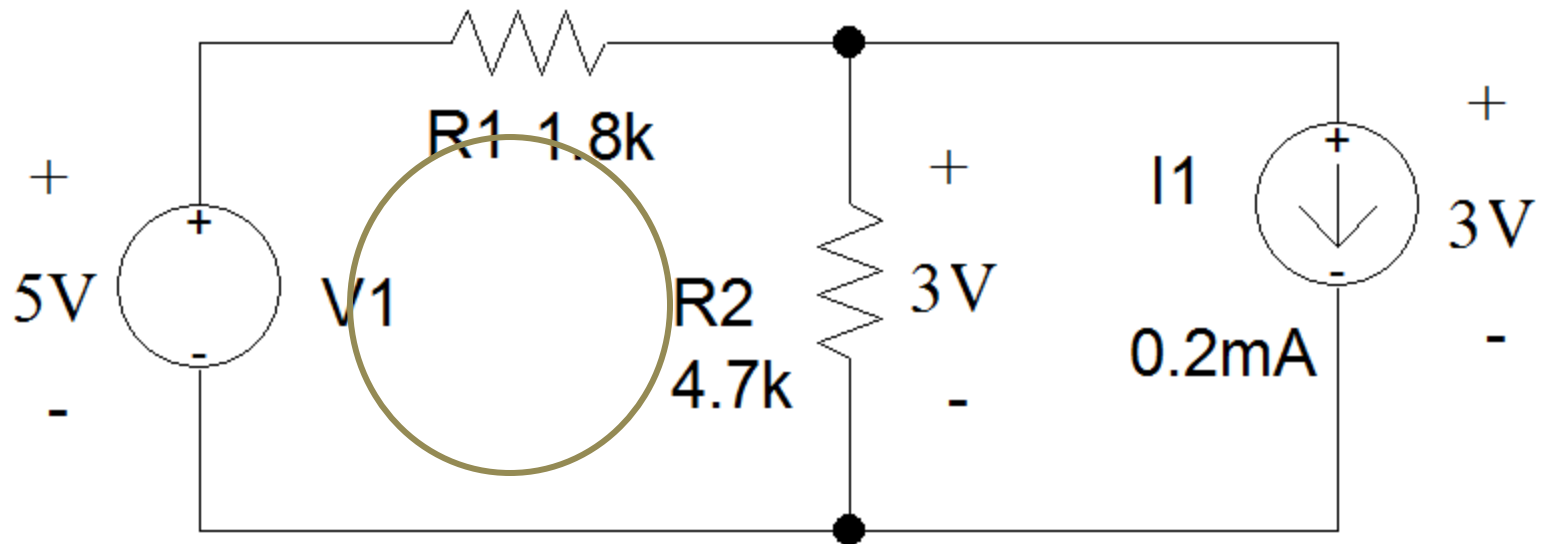


# Example 4 (con't)

- As should happen, the answer is the same.

$$-5V - V_{R1} + 3V = 0$$


$$V_{R1} = -2V$$

$$- V_{R1} +$$

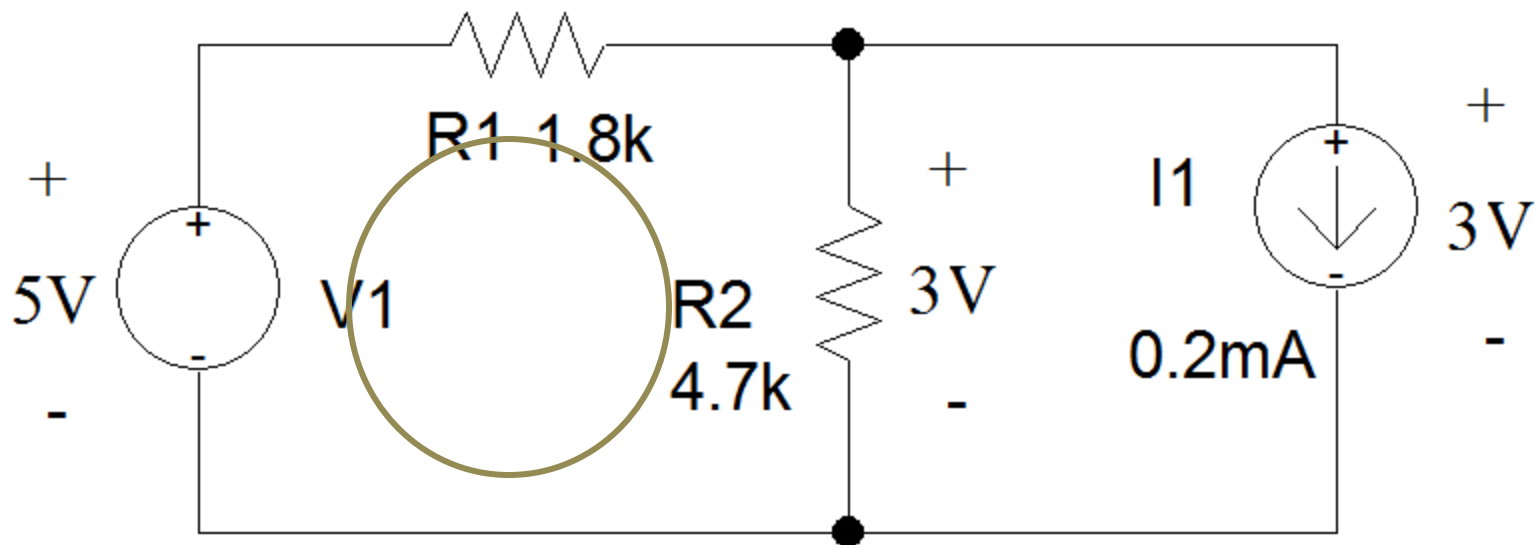

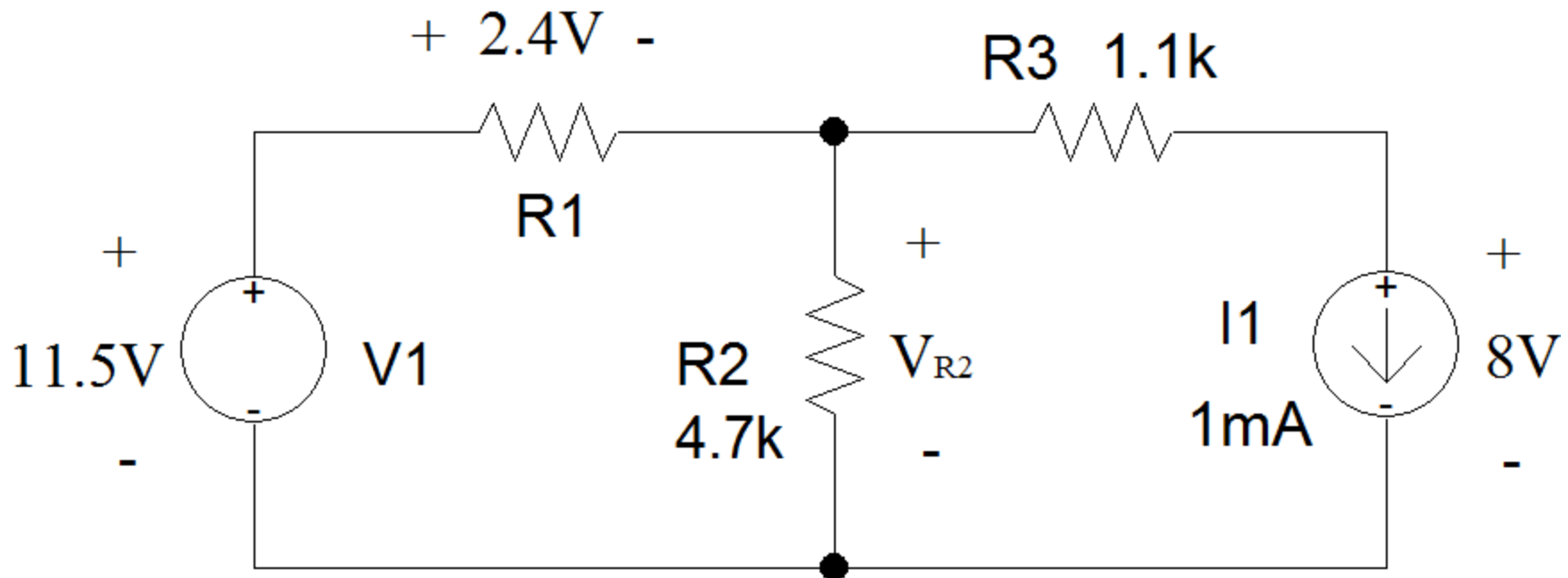
# Example 5

- Find the voltage across  $R_2$  and the current flowing through it.
  - First, draw a loop that includes  $R_2$ .



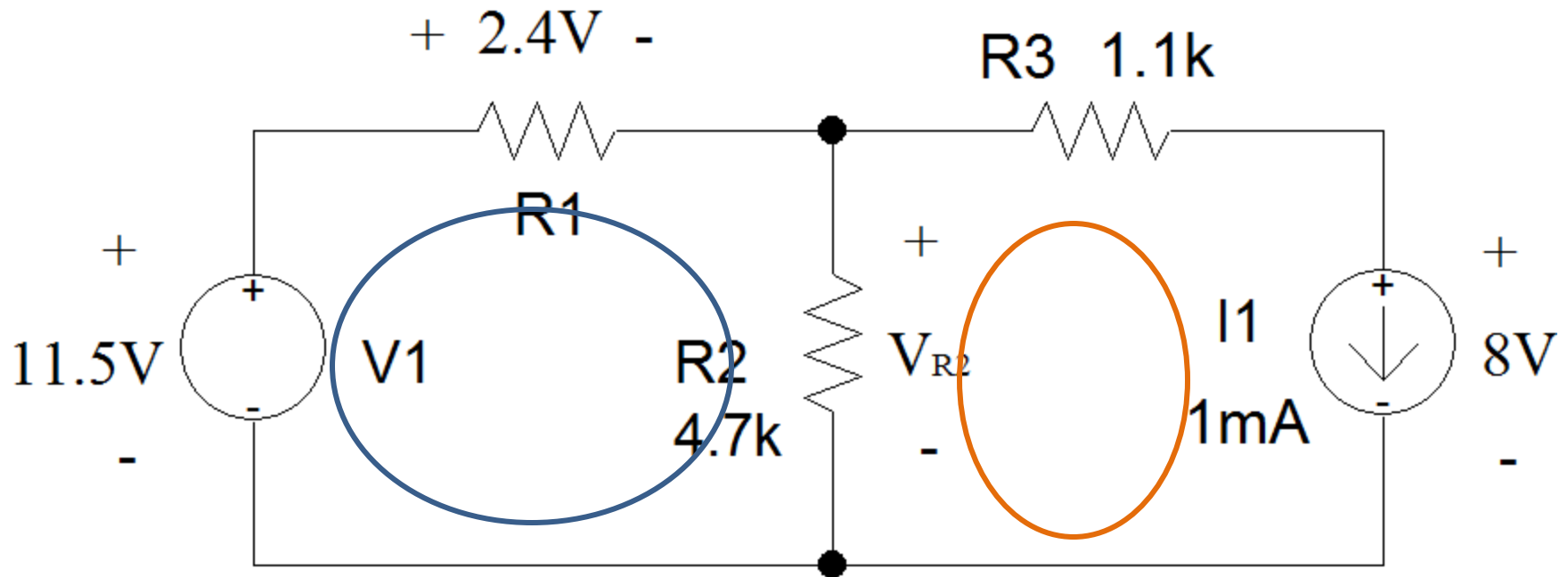
# Example 5 (con't)

- There are two loops that include  $R_2$ .
  - The one on the left can be used to solve for  $V_{R_2}$  immediately.


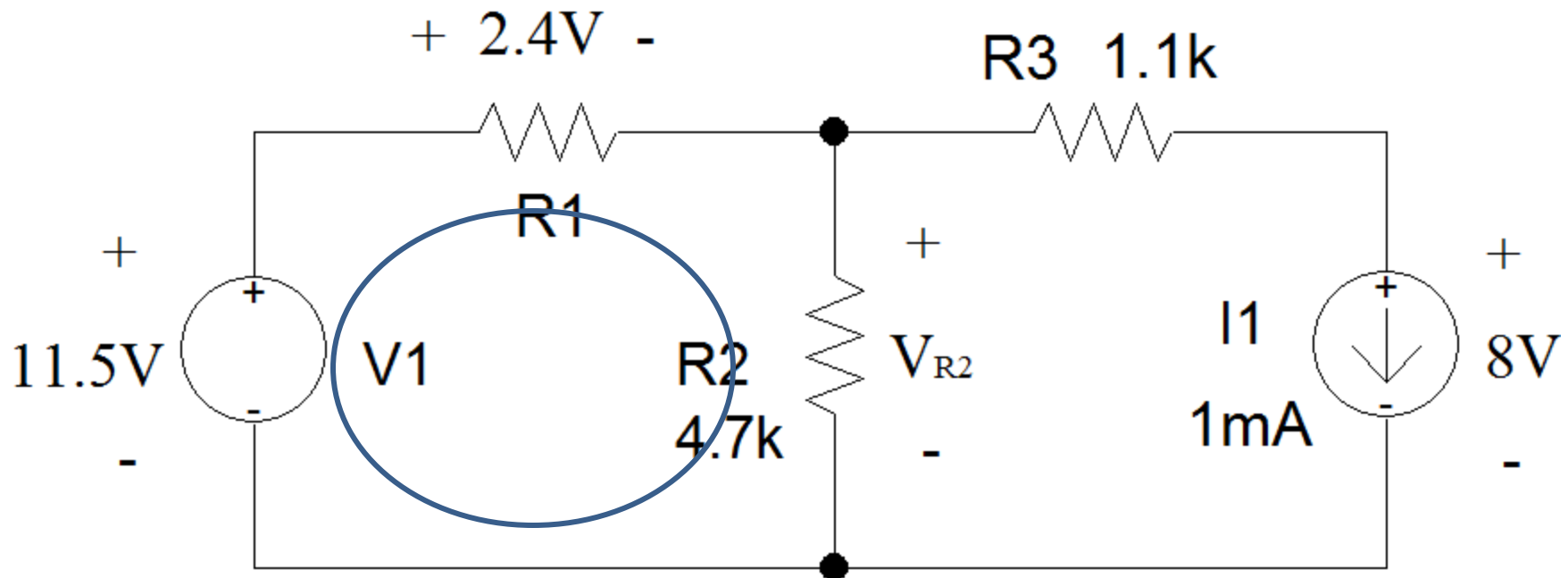
# Example 5 (con't)

- Following the loop in a clockwise direction.
  - The 11.5V drop associated with V1 is a voltage rise.
  - The 2.4V associated with R1 is a voltage drop.
  - $V_{R2}$  is treated as a voltage drop.






# Example 5 (con't)


$$-11.5V + 2.4V + V_{R2} = 0$$

$$V_{R2} = 9.1V$$

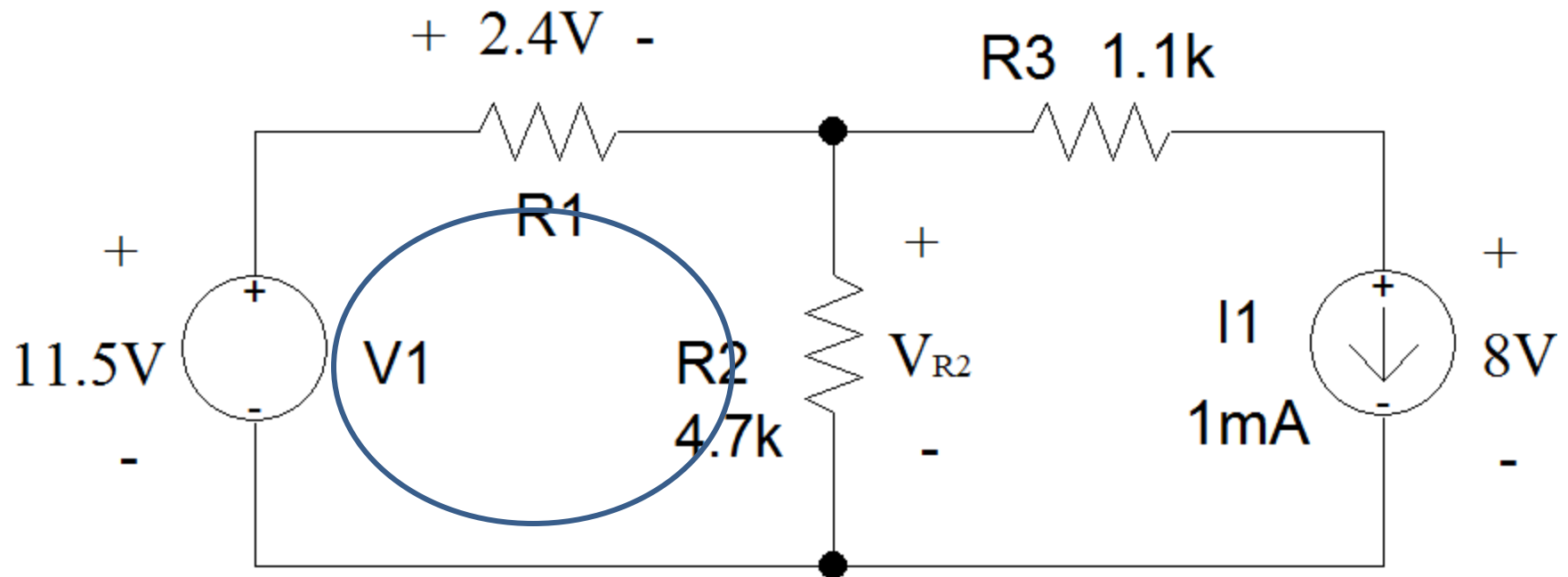
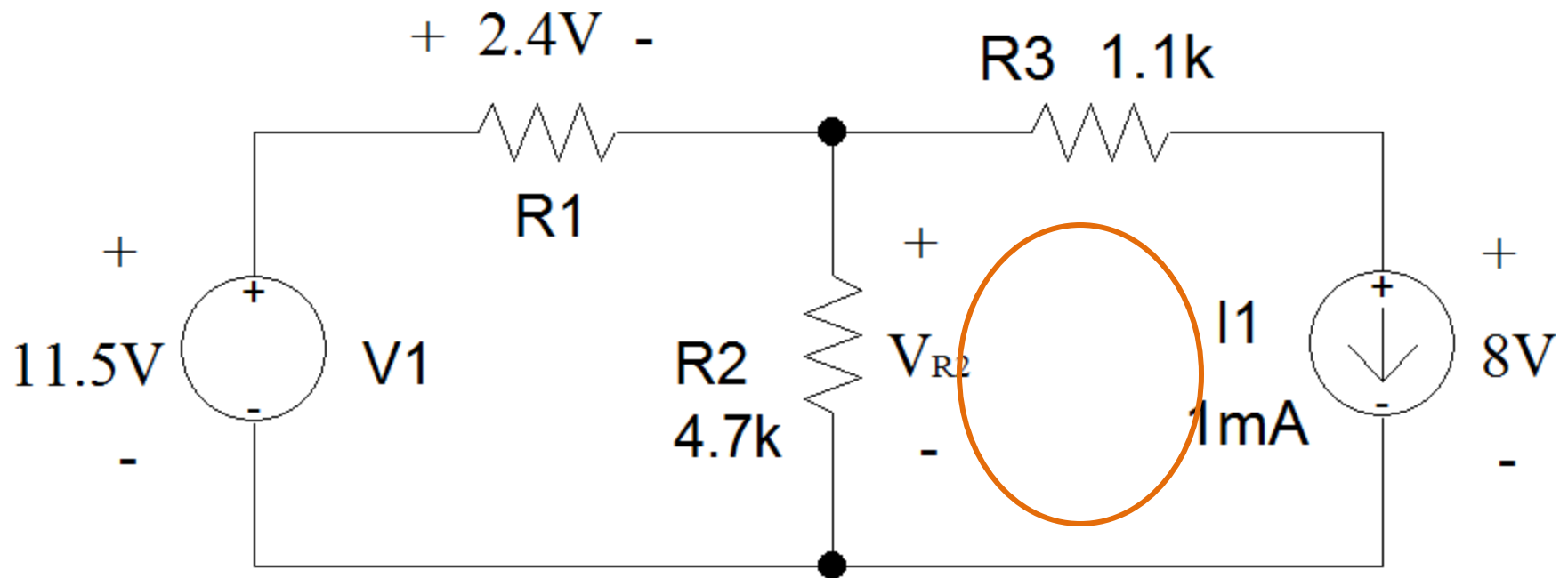
# Example 5 (con't)

- If you used the right-hand loop, the voltage drop across  $R_3$  must be calculated using Ohm's Law.




# Example 5 (con't)

- Since  $R_3$  is a resistor, passive convention means that the positive sign of the voltage drop will be assigned to the end of  $R_3$  where current enters the resistor.
- As  $I_1$  is in series with  $R_3$ , the direction of current through  $R_3$  is determined by the direction of current flowing out of the current source.
- Because  $I_1$  and  $R_3$  are in series, the magnitude of the current flowing out of  $I_1$  must be equal to the magnitude of the current flowing out of  $R_3$ .

# Example 5 (con't)


- Use Ohm's Law to find  $V_{R3}$ .

$$V_{R3} = 1mA(1.1k\Omega) = 1.1V$$

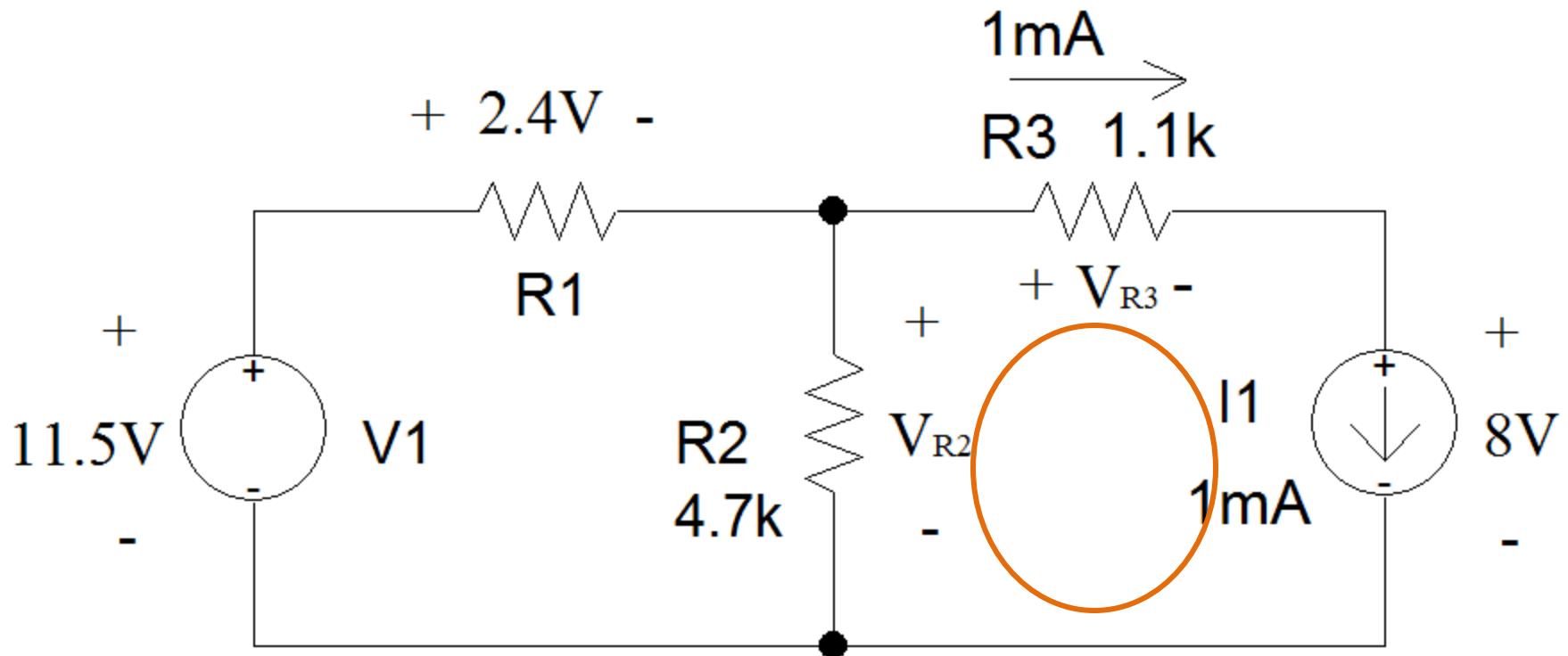
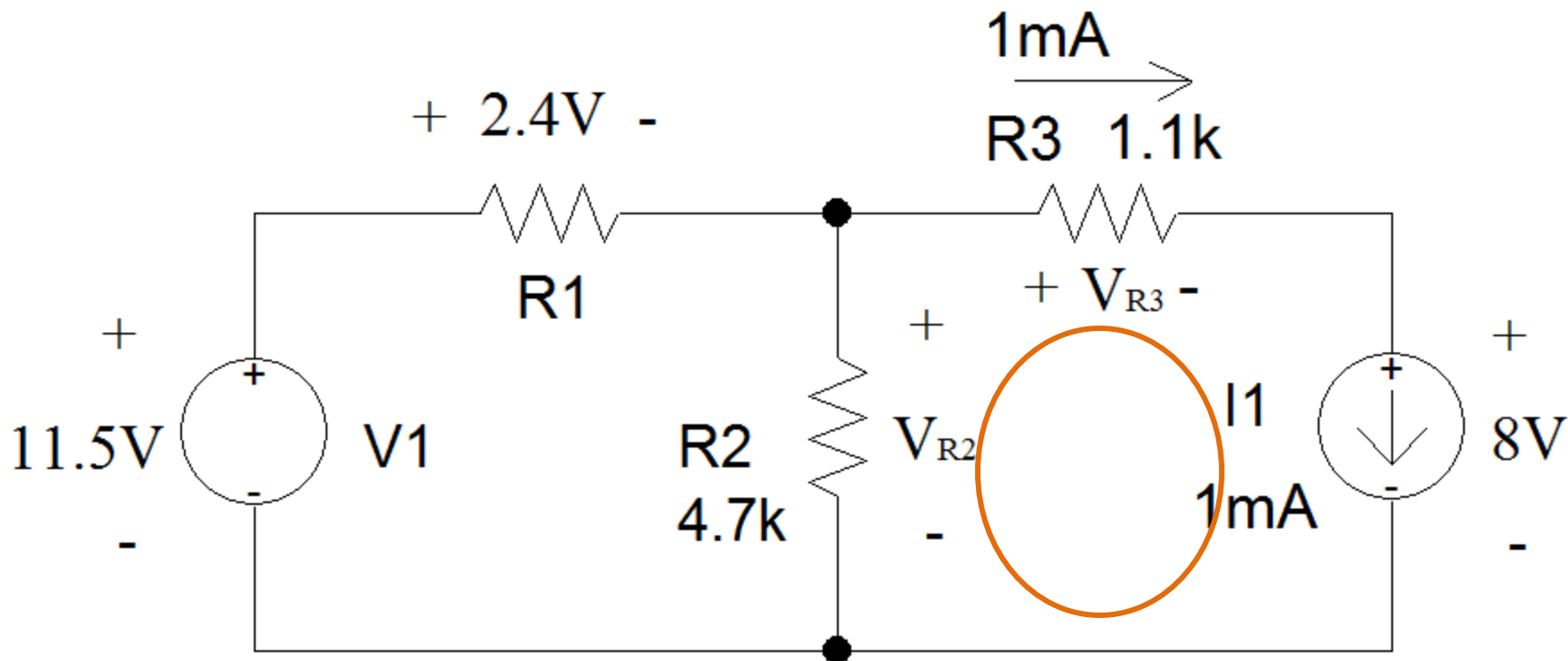
# Example 5 (con't)

- Moving clockwise around the loop:
  - $V_{R3}$  is a voltage drop.
  - The voltage associated with  $I1$  is a voltage drop.
  - $V_{R2}$  is a voltage rise.




# Example 5 (con't)

Again, the same answer is found.

$$1.1V + 8V - V_{R2} = 0$$


$$V_{R2} = 9.1V$$

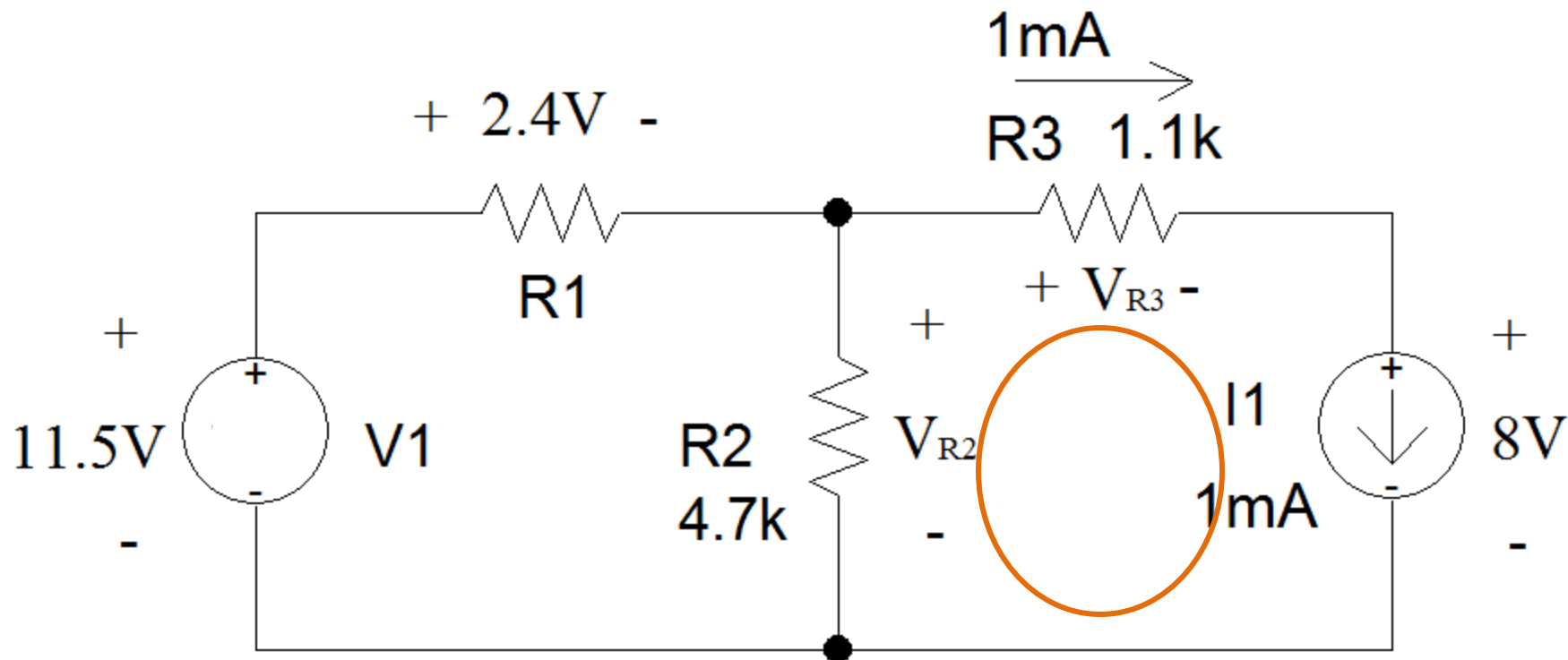
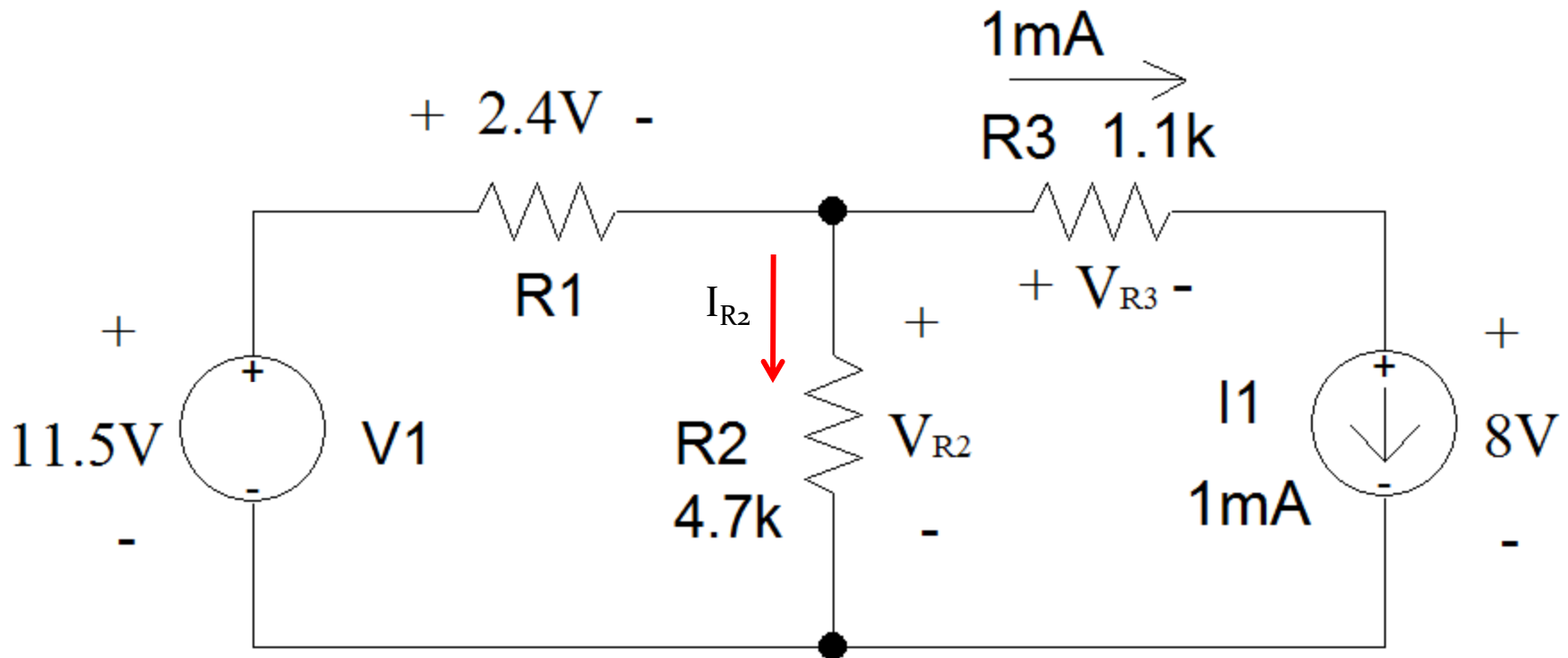
# Example 5 (con't)

Once the voltage across  $R_2$  is known, Ohm's Law is applied to determine the current.

The direction of positive current flow, based upon passive sign convention is shown in red.



# Example 5 (con't)

$$I_{R2} = 9.1V / 4.7k\Omega$$

$$I_{R2} = 1.94mA$$

