

MICROPROCESSOR SYSTEMS
Visa Exam

8th / April / 2004

1- Calculate the value of A (Accumulator) by using hexadecimal number system at the end of following series of logical operations. (Please, write the results in a box)

a) MOV A,#75H ; A=(75)₁₆
 ANL A,#00001111B
 XRL A,#0FH ; $\Rightarrow A = (???)_{16}$


b) MOV A,#1H ; A=(1)₁₆
 MOV R1,#10D
LOOP2: MOV R0,#3D
LOOP1: ADD A,R0
 DJNZ R0,LOOP1
 DJNZ R1,LOOP2

 ; $\Rightarrow A = (???)_{16}$

2- In a 64Kbyte memory system, most significant 4bits of the address lines are connected to the activation inputs (\overline{CE}) of the memory components through a 4x3 decoder.

- a) Draw the component activation table (Logical truth table of the decoder) with respect to memory component activation addresses listed below
0000H-1FFFH Device connected at $\overline{Y0}$ will be active (Active low)
2000H-9FFFH Device connected at $\overline{Y1}$ will be active (Active low)
A000H-AFFFH Device connected at $\overline{Y2}$ will be active (Active low)

 - b) Find the minimized logical expressions of the outputs $\overline{Y0}$, $\overline{Y1}$ and $\overline{Y2}$
c) Draw the related logical circuit schema using the TTL gates given in the datasheet



3- An 8 bit CPU having 64Kbytes addressing capability will be connected to a memory block containing 1 piece of 27C64 EPROM, 1 piece of 62C128 static RAM, 1 piece of 28C64 EEPROM and an address decoder unit. EPROM will contain the program memory and the initial address after the reset indicates first address of this device (0000H)

- a) Give the outline of the memory organization map
b) Draw the circuit schema of the memory block and the related memory-addressing map of the described system using 74HC138 as decoder.

Total time : 95minutes

Suggested timing : 1-a)5m b)10m 2-a)10m b)20m c)15m 3-a)10m b)25minutes

1- a)10P b)15P 2- a) 10P b) 20 c)10 P 3-a)10 b) 25 Points